

VE527

Computer-Aided Design of Integrated Circuits


Static Timing Analysis; Interconnect Modeling

Outline

- Static Timing Analysis: Algorithm
- Interconnect Timing
 - Electrical Models of Wire Delay
 - Elmore Delay Model

The Most Typical STA Problem

 - Answer this problem: What are all the too-slow paths that violate timing?
- Most useful report:
 - Report paths **in order**, from slowest to fastest.
 - In other words: **Enumerate** these paths, in delay order.




What Do We Need?

- Calculate all the **ATs**.
- Calculate all the **RATs**.
- Calculate all the **Slacks**.
- ... do all of these very **efficiently**: Delay graphs are huge!
- **Enumerate** the violating paths, in worst delay order.

Computational Strategy

 - **Topological sorting** (“**Topsorting**”) the delay graph.
 - Sort the vertices in the delay graph into one single ordered list.
 - Essential property: if there is an edge from p to s , then p appears before s in sorted order.
- Compute ATs by going **forward** through the sorted list.
- Compute RATs by going **backward** through the sorted list.




Legal Topsorting Order

a, b, c, d, e, f

a, b, d, c, e, f

Compute ATs

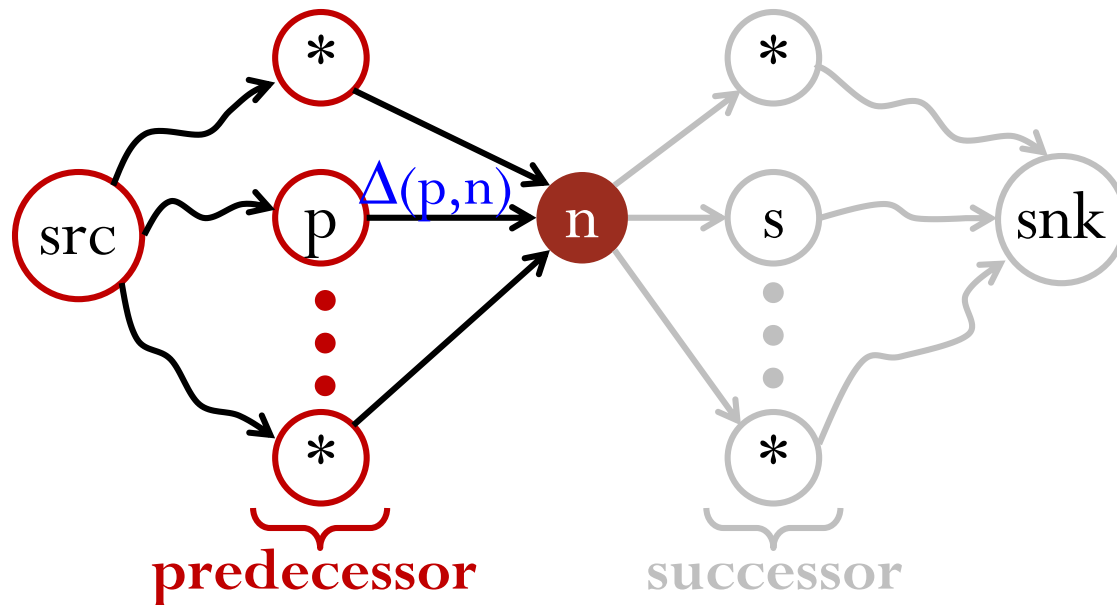
```
computeATs() {  
  AT(SRC) = 0;  
  foreach ( n in topsort order ) {  
    AT(n) =  $-\infty$ ;  
    foreach ( node p in pred(n) )  
      AT(n) = max( AT(n), AT(p) +  $\Delta(p,n)$  );  
  }  
}
```



Compute RATs


- Pretend all edges are **reversed**, they point from SNK to SRC, and walk graph **backwards**.
 
```
computeRATs() {  
  RAT(sink) = CycleTime;  
  foreach ( n in reverse topsort order ) {  
    RAT(n) =  $\infty$ ;  
    foreach (successor s in succ(n) )  
      RAT(n) = min( RAT(n), RAT(s) -  $\Delta(n,s)$  );  
  }  
}
```




Path Reporting

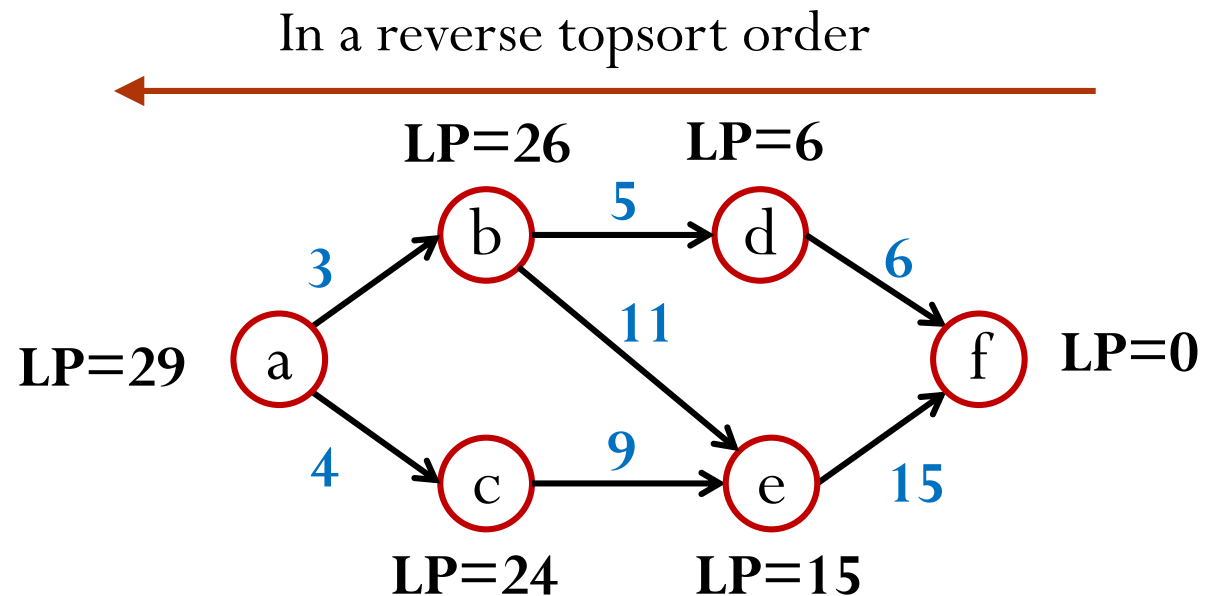- If only the longest path, can use slack property: all nodes on longest path have **same worst slack value**.
- How can we find **N worst (longest) paths**?
 - We will use **longest path (LP) to sink** for each node (related to **RAT**)



N-Worst Path Reporting

 - We evolve **partial paths**; each partial path stores 3 things:
(Path itself, Delay of this path, Max delay **through** this partial path to sink)
 - Max delay through this partial path to sink = Delay of this path + longest path (LP) from last node on the path to sink




Consider partial path (a,b).
Max delay through it = $3 + 26 = 29$

N-Worst Path Reporting

- We store the partial paths in a **max heap**, which is indexed on the last entry, max delay through the path (i.e., delay+LP).
- Initially this heap contains only the **source node**.
- Algorithm is quite simple (and just like maze routing!).
 - **Expand**: Pop the partial path has the largest last entry off the heap
 - Reach target? If its end node is the sink, print out the path
 - **Reach**: Else add each **successor** node to make **new** partial paths, push them back onto the heap, each with (Path, Delay, Delay+LP) labeled.
- Go pop next partial path until N paths are reported.

Worst Case Path Reporting: Example

 

- Max heap entry of the form (Path, Delay, Delay+LP)
 - Initially, heap contains only the **source node**.

Max Heap


(a,0,29)

Expand path a,
reach b & c

Max Heap

(a-b,3,29)
(a-c,4,28)

Worst Case Path Reporting: Example

 

Max Heap


(a-b, 3, 29)
(a-c, 4, 28)

Expand path a-b,
reach d & e

Max Heap

(a-b-e, 14, 29)
(a-c, 4, 28)
(a-b-d, 8, 14)

Worst Case Path Reporting: Example

 

Max Heap

(a-b-e, 14, 29)
(a-c, 4, 28)
(a-b-d, 8, 14)


Expand path a-b-e,
reach f

f is **sink**! Report 1st
worst path a-b-e-f,
with delay=29

Max Heap

(a-c, 4, 28)
(a-b-d, 8, 14)

Worst Case Path Reporting: Example

 

Max Heap


(a-c, 4, 28)
(a-b-d, 8, 14)

Expand path a-c,
reach e

Max Heap

(a-c-e, 13, 28)
(a-b-d, 8, 14)

Worst Case Path Reporting: Example

 

Max Heap

(a-c-e, 13, 28)
(a-b-d, 8, 14)


Expand path a-c-e,
reach f

f is **sink**! Report 2nd
worst path a-c-e-f,
with delay=28

Max Heap

(a-b-d, 8, 14)

Worst Case Path Reporting: Example

 

Max Heap

(a-b-d, 8, 14)

Expand path a-b-d,
reach f


f is **sink**! Report 3rd
worst path a-b-d-f,
with delay=14

Max Heap

(EMPTY)

Done!

Worst Case Path Reporting: Example

 

- We find three paths:
 - a-b-e-f, delay = 29
 - a-c-e-f, delay = 28
 - a-b-d-f, delay = 14.

Note: only 3 possible paths from source to sink in graph, so we found them correctly in **delay order**!

Static Timing Analysis: Summary

- STA is a **very important** step in design of complex ASICs.
 - It's a critical “**sign off**” step, which means: you don't get to fabricate unless you pass.
- Several big ideas
 - **Gate level delay** models matter, and can be pretty complex in real world.
 - Logical \neq Topological path analysis (i.e., STA).
 - Build **delay graph**, calculate **ATs**, **RATs**, **slacks** recursively.
 - Concept of **slack** is **important**: lets us locate worst paths, and problem gates on path.
 - A similar idea to maze routing lets us find **worst paths in delay order**.

Static Timing Analysis: Aside


- STA is a **huge** topic – several things we did not cover.
- **STA for sequential elements**
 - How do we model flip flops and latches, so we can verify, e.g., that setup and hold times are met? More tricks with delay graph.
- **Early mode versus late mode timing**
 - Our development was only so-called **late mode** timing, where we care about longest path. **Early mode** focuses on shortest paths, and is critical for more advanced timing.
- **Incremental STA**
 - In practice, you change 10,000 gates out of 1,000,000 gates, you don't want to **redo** the whole STA analysis. Advanced methods can update **incrementally**.

Outline

- Static Timing Analysis: Algorithm
- Interconnect Timing
 - Electrical Models of Wire Delay
 - Elmore Delay Model

Interconnect (Wire) Delay Modeling

 
- You place the logic. Pins are put at a certain distance apart.
- You route the wires. Each wire has an input-to-output **delay**.
- Questions:
 - Where does the delay come from?
 - How **accurately** can we **predict** this delay?
 - How **efficiently** can we **model** this delay for use in layout synthesis or STA?



Delay!


Interconnect Model

 - We model interconnect as an **electrical circuit** and analyze it as a circuit.
- The model parameters depend critically on **exact geometry** of the wired net.
- Most popular interconnect model used in layout applications: **RC trees**.




Interconnect Model: Resistance

 - Metal wire has **resistance R** to current flowing down its length.
- **In physics:** $R = \frac{\rho L}{S} = \frac{\rho L}{WH}$
- **In ASIC design:** H is a manufacturing factor. Only W and L can be controlled $\Rightarrow R = \frac{rL}{W}$



Interconnect Model: Capacitance

 - Metal wire has **capacitance C** to silicon substrate, with insulator between.
- **In physics:** $C = \frac{\epsilon WL}{d}$
- **In ASIC design:** d is a manufacturing factor. Only W and L can be controlled $\Rightarrow C = cWL$




Aside: About Real Capacitance (Cap)

- Note: this model is very **simplistic**.
- You really get capacitance between **any pair of conducting surfaces**.
 - So, in a multi-layer metal process you get caps **between all the layers**.

Overlap cap

 between 2 adjacent wires on different layers



Sidewall fringe cap


from side of one layer to the conductors below it

Fringe cap

between 2 adjacent wires on the same layers.


Typical Interconnect Model: π Model

 - Accounts for the resistance R and the capacitance C of wire segment.
- It is a **small** model: only need 2 numbers.
- It is a **symmetric** model: **split** capacitance into two halves.






From Wire Segments to RC Tree

 - Big idea: Replace **every** straight wire segment with π model.




From Wire Segments to Final RC Tree

   - Simplification: Recall a rule from basic circuits:
 - **Parallel** capacitors can be replaced by 1 capacitor with ΣC_i




General Form of RC Tree

 - Capacitors “**hanging off**” all tree nodes.
- Tree edges are **resistors**.
- **Root** of tree is where signal is input.
- **Leaves** of tree are the driven outputs.




Model the Driving and Driven Gates

 - We also need to model **driving gate** and **driven gates**.
 - **Voltage source** + **resistor** as input at root. This models **driving gate**.
 - **Capacitor** as load at each leaf. Each models a **driven gate**.



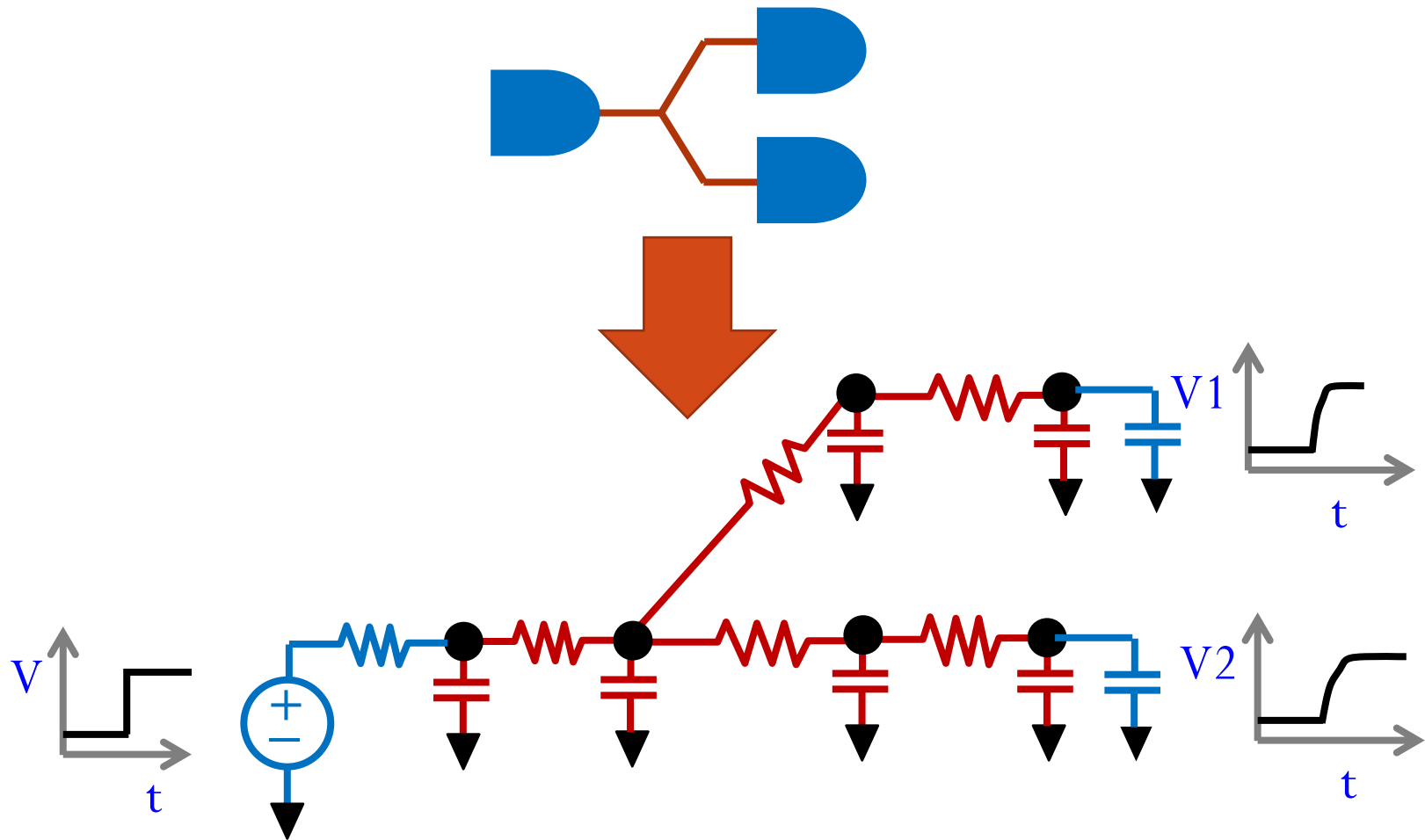Summary: RC Tree Is Built from Gates + Wires




Outline

- Static Timing Analysis: Algorithm
- Interconnect Timing
 - Electrical Models of Wire Delay
 - Elmore Delay Model

Calculating Delay

 
- How to calculate a **delay** number for **each output** of tree?
- Famous formula: **“Elmore” delay**
 - Derived in 40s for circuits applications.
 - Resurrected in 80s by Penfield et al. for RC trees.
 - A very **simple**, but very **useful** computational recipe.



Elmore Delay τ :

Tree Walk Computing Recipe

 
- Set $\tau = 0$. Walk down path of resistors from **Root** to **Leaf** where you want to calculate delay.
- At each resistor, let
$$\tau = \tau + R \cdot \Sigma \text{ (all capacitors downstream)}$$
 - **Downstream capacitor** = any C that is reachable in tree below this resistor.



 Example: at $R2$ resistor in RC tree, the downstream capacitors are, 2, 1, 1, 3, 1

Calculating Elmore Delay: Example


- Set $\tau = 0$. Walk down path of resistors from **Root** to **Leaf** where you want to calculate delay.
- At each resistor, let $\tau = \tau + R \cdot \Sigma$ (all capacitors downstream)




$$\begin{aligned}
 \tau &= 0 \\
 &+ 5 \times (1 + 2 + 1 + 3 + 1 + 1) \\
 &+ 2 \times (2 + 1 + 3 + 1 + 1) \\
 &+ 4 \times (1 + 3) \\
 &+ 1 \times 3 \\
 &= 45 + 16 + 16 + 3 \\
 &= 80
 \end{aligned}$$

Insight: Stream Analogy

 - Think of RC tree like **branching stream**, current like **water**.
 - Goal: You are downstream, trying to fill your bucket. How **fast** can you fill it?
 - However, at **every** branch point, somebody else has a **bucket**.
 - The **farther** you are downstream, the **less** water you get from upstream.
- What matters here?
 - **Width** of the upstream branches.
 - **Size** of all the buckets.




From Stream to Circuit

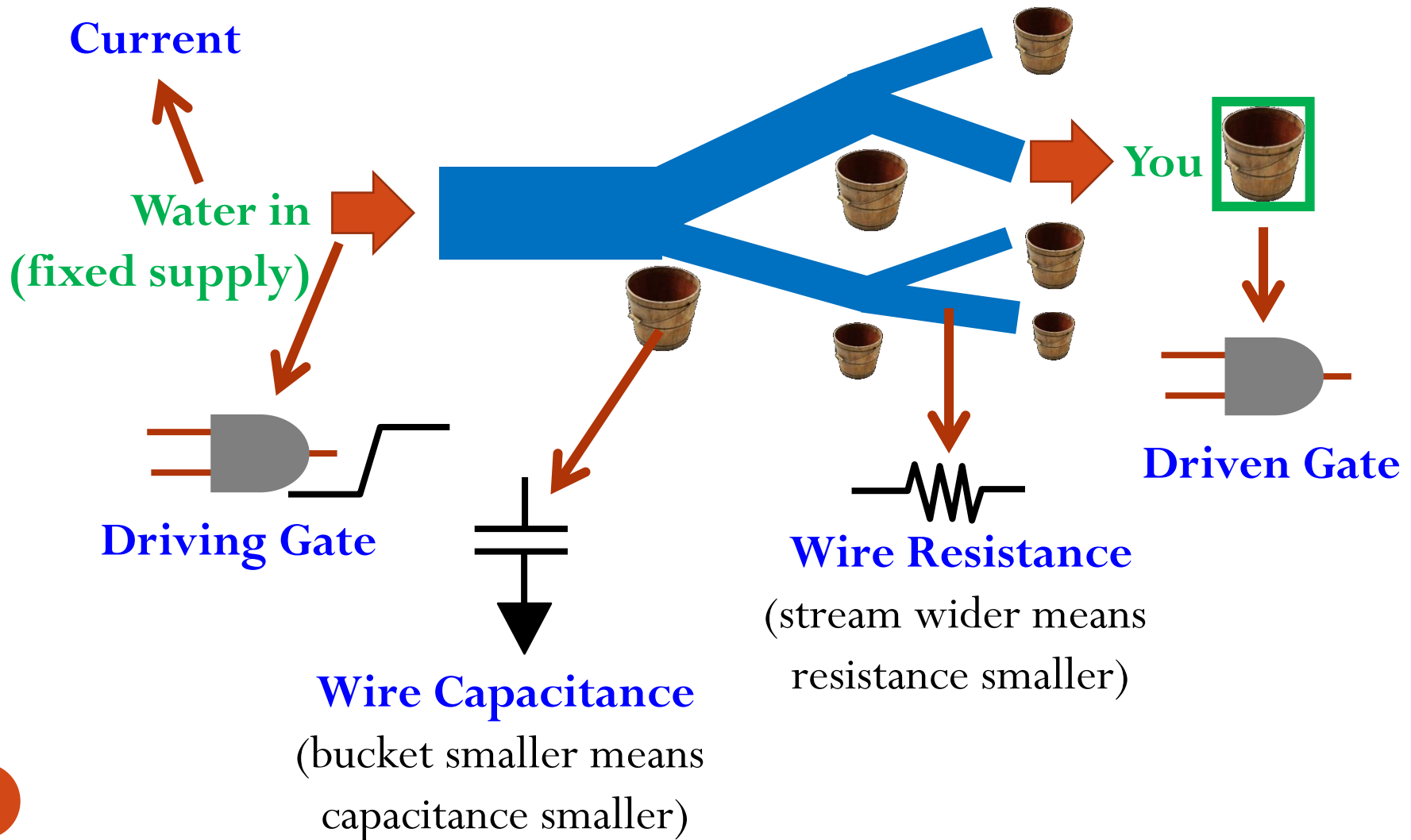


Circuit Aside: What Is Elmore Delay?

 - If you want to model the path from input to an output as a simplified circuit with **exactly one** R and **one** C, the **best approximation** you have will have its $R \cdot C =$ Elmore delay.
 - Note: for a circuit with one R and one C, $R \cdot C$ is the **time constant** τ .




 Elmore delay is the time constant of the best approximating circuit with one R and one C




Elmore Delay Example

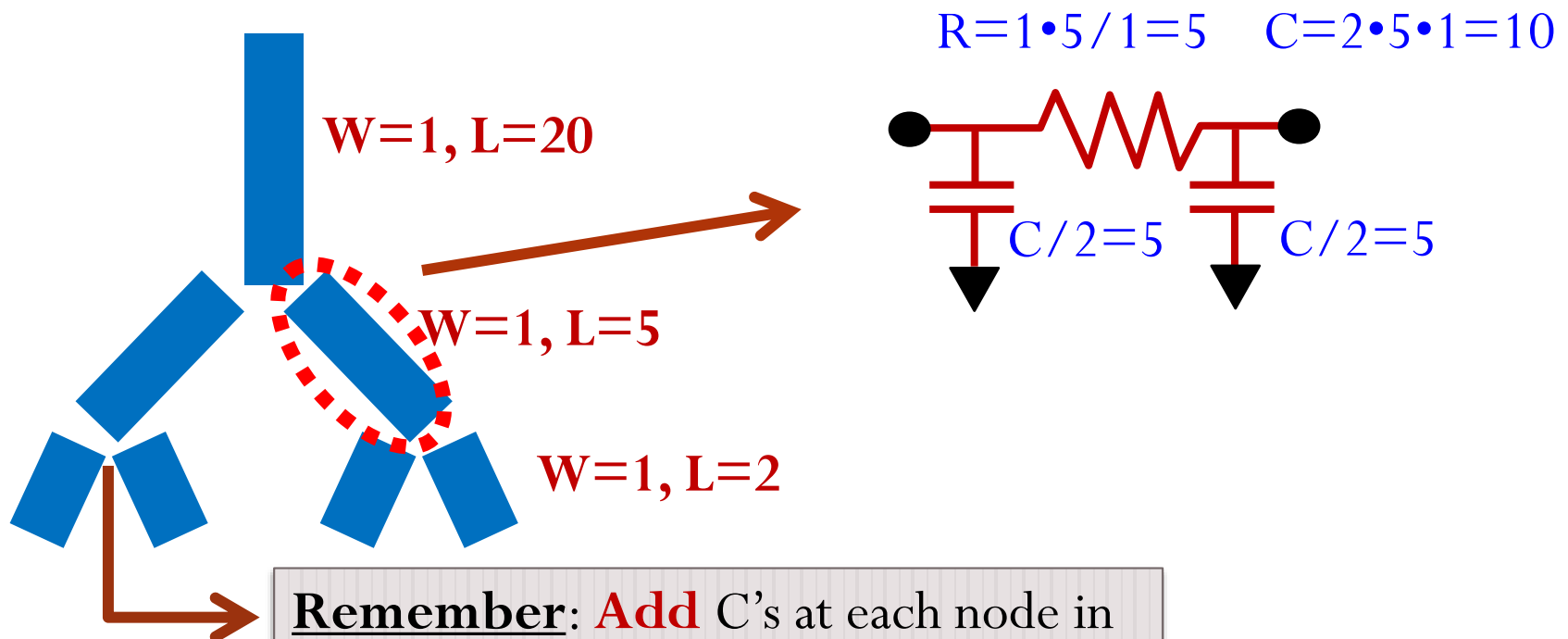- Simple tree with 4 leaf nodes
 - For each segment, total $R=rL/W$, $C=cWL$.
 - Electrical parameters: $r=1$, $c=2$.




Elmore Delay Example

 - RC Tree for the interconnect alone
 - Remember to add up C's hanging off each internal node of tree




Elmore Delay Example

- Add driver and driven gates

 

Elmore Delay Example

 - Now we can compute delay to each leaf.
- Since symmetric, only need to compute 1 path.




Remember the recipe:

1. Set $\tau = 0$, walk from root to leaf
2. At each R,
 $\tau += R \cdot \Sigma$ (all C's downstream)

$$\begin{aligned}
 \tau &= 0 \\
 &+ 20 \times (20 + 30 + 2 \times 9 + 4 \times 3) \\
 &+ 20 \times (30 + 2 \times 9 + 4 \times 3) \\
 &+ 5 \times (9 + 2 \times 3) \\
 &+ 2 \times 3 \\
 &= 2881
 \end{aligned}$$

Elmore Delay Applications

 - Timing verification
 - Can use this to give realistic post-layout **wire delays** for final STA.



Elmore Delay Applications

- During placement
 - Estimate **wire shape** (e.g., a simple Steiner tree), then you can get **very quick** delay estimate.
 - Analytical placers use to adjust **weights** on wires, force critical wires to be **short**.

Summary

- Interconnect has a **huge** impact on chip speed.
 - Cannot ignore delays caused by the electrical properties of real wires
- Individual wires are today modeled as complex circuits.
 - RC tree is the most useful model; Elmore delay is easiest to compute
 - Can use for both verification, and for layout optimizations
 - Accurate enough that they beat simple length-based schemes.
 - Unfortunately, not so accurate that you can avoid later verification with “**higher order**” models that incorporate **more than one** time constant.
 - There are sophisticated estimators beyond Elmore, but they takes more time.