

VE527

Computer-Aided Design of Integrated Circuits

Multi-Level Logic Synthesis:
Don't Cares

Outline


- Implicit Don't Cares
 - Introduction
 - Method to Obtain them

Don't Cares

- We made progress on multi-level logic by **simplifying** the model.
 - Algebraic model: we **get rid of** a lot of “difficult” Boolean behaviors.
 - But we lost some optimality in the process.
- How do we put it back? One surprising answer: **Don't cares**
 - To help this, **extract** don't cares from “surrounding logic,” use them **inside each node**.
- The big difference in multi-level logic
 - Don't cares happen as a natural byproduct of Boolean network model: called **Implicit Don't Cares**.
 - They are all over the place, in fact. Very useful for simplification.
 - But they are **not explicit**. We have to **go hunt for them**...

Don't Cares Review: 2-Level

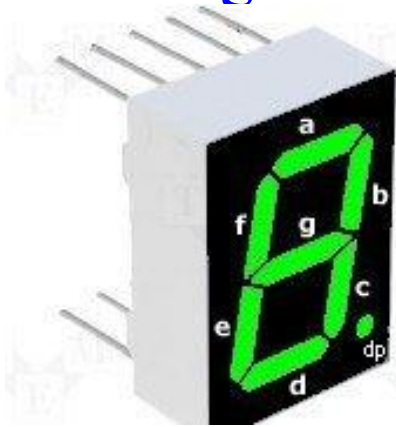- In basic digital design...
 - Don't Care (DC) = an input pattern that **can never happen** or you don't care the output if it happens.
 - Example: use **binary-coded decimals (BCD)** to control **seven-segment digital tube**.



How about input (x,y,z,w)
 $= (1,0,1,0), (1,0,1,1) \dots?$

Don't care!

x y z w	decimal value	segment a
0 0 0 0	0	1
0 0 0 1	1	0
0 0 1 0	2	1
0 0 1 1	3	1
0 1 0 0	4	0
0 1 0 1	5	1
0 1 1 0	6	1
0 1 1 1	7	1
1 0 0 0	8	1
1 0 0 1	9	1

Don't Cares Review: 2-Level

- Since patterns $(x,y,z,w)=(1,0,1,0), (1,0,1,1), (1,1,0,0), (1,1,0,1), (1,1,1,0), (1,1,1,1)$ are don't cares, we are **free to decide** whether $F=1$ or 0 , to better **optimize** F .

x y z w	decimal value	segment a
0 0 0 0	0	1
0 0 0 1	1	0
0 0 1 0	2	1
0 0 1 1	3	1
0 1 0 0	4	0
0 1 0 1	5	1
0 1 1 0	6	1
0 1 1 1	7	1
1 0 0 0	8	1
1 0 0 1	9	1


		xy			
		00	01	11	10
zw	00	1	0	d	1
	01	0	1	d	1
	11	1	1	d	d
	10	1	1	d	d

Don't Cares (DCs): Multi-level

- What's different in multi-level?
 - DCs arise **implicitly**, as a result of the **Boolean logic network structure**.
 - We must go find these implicit don't cares — we must search for them explicitly.

Multi-level DCs: Informal Tour

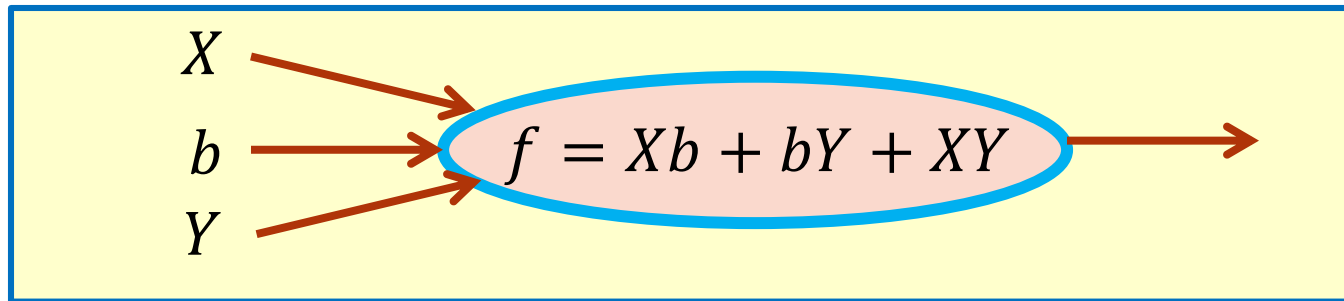
- Suppose we have a Boolean network and a node f in the network.



- Can we say anything about **don't cares** for node f ?
 - No. We don't know any "context" for surrounding parts of network.
 - As far as we can tell, all patterns of inputs (X, b, Y) are possible.
 - We **cannot further simplify** the expression for f .


Multi-level DCs: Informal Tour

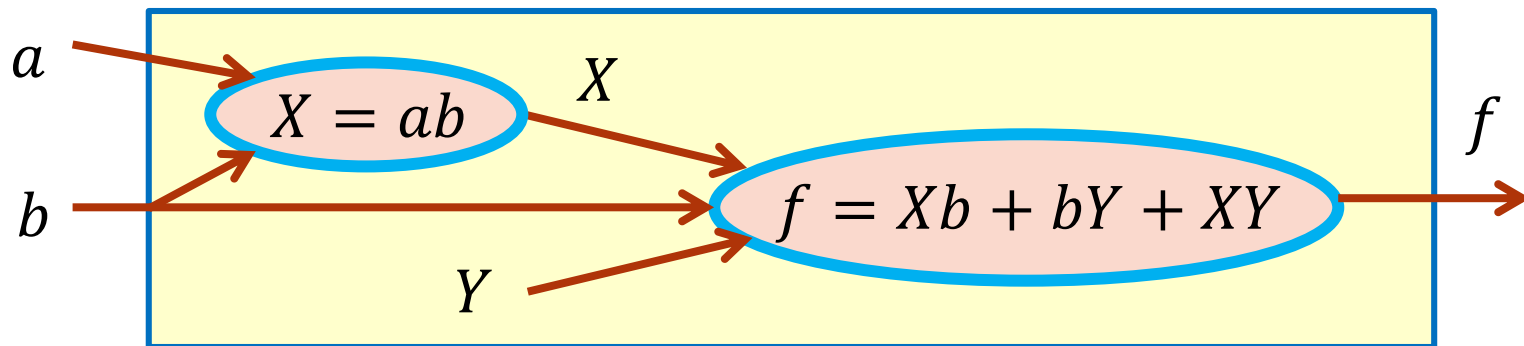- Now suppose we know something about input X to f :
 - Node $X = ab$.
 - Also assume a and b are **primary inputs (PIs)** and f is **primary output (PO)**.



- Now can we say something about DCs for node f ...?
 - **YES!**
 - Because there are some **impossible patterns** of (X, b, Y) .

Multi-level DCs: Informal Tour

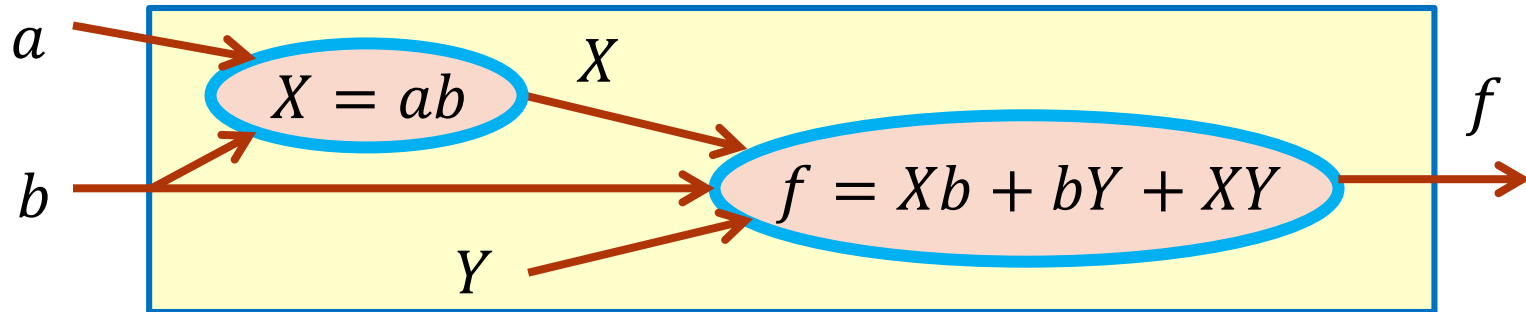

The possible input/output patterns for node X


a	b	X	Can it occur?
0	0	0	Yes
0	0	1	No
0	1	0	Yes
0	1	1	No
1	0	0	Yes
1	0	1	No
1	1	0	No
1	1	1	Yes



b	X	Can it occur?
0	0	Yes
0	1	No
1	0	Yes
1	1	Yes

Impossible patterns for (X, b, Y) are:
 $(1, 0, 0)$ and $(1, 0, 1)$

Multi-level DCs: Informal Tour

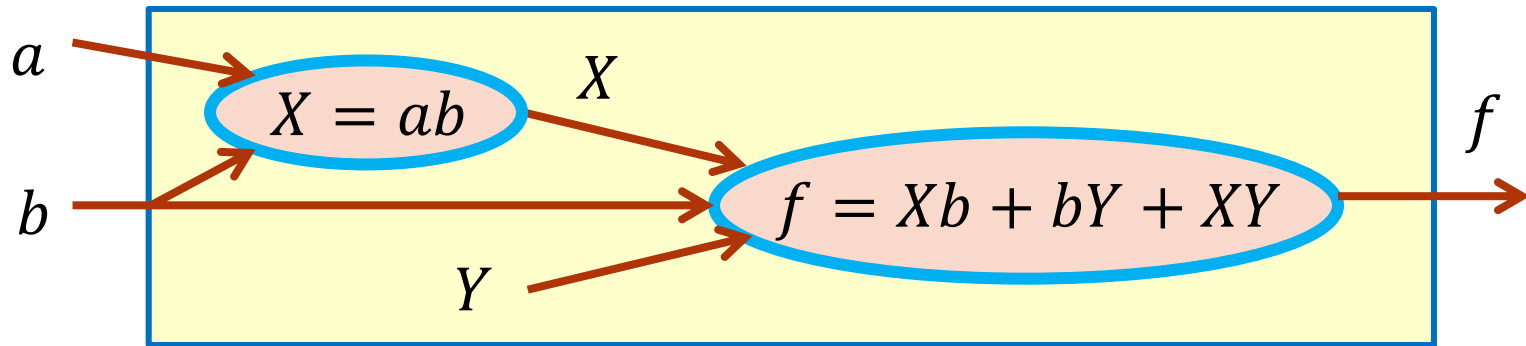

- Impossible patterns for (X, b, Y) are $(1, 0, 0)$ and $(1, 0, 1)$.
 - With them, we can simplify f .

Can be simplified as
 $f = X + bY$

Kmap for $f = Xb + bY + XY$


Xb					
Y		00	01	11	10
	0			1	
	1		1	1	1

With don't
cares


Xb					
Y		00	01	11	10
	0			1	d
	1		1	1	d

Multi-level DCs: Informal Tour

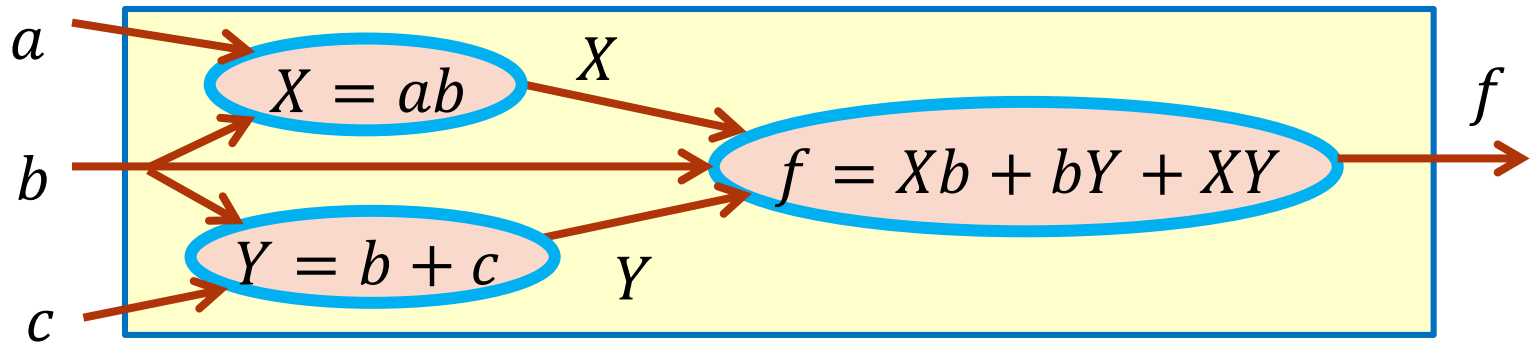- Now further suppose $Y = b + c$. What will happen?




b	c	Y	Can it occur?
0	0	0	Yes
0	0	1	No
0	1	0	No
0	1	1	Yes
1	0	0	No
1	0	1	Yes
1	1	0	No
1	1	1	Yes

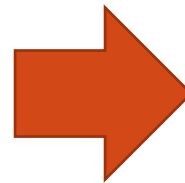

b	Y	Can it occur?
0	0	Yes
0	1	Yes
1	0	No
1	1	Yes

Impossible patterns for (X, b, Y) are:
 $(0, 1, 0)$ and $(1, 1, 0)$

Multi-level DCs: Informal Tour

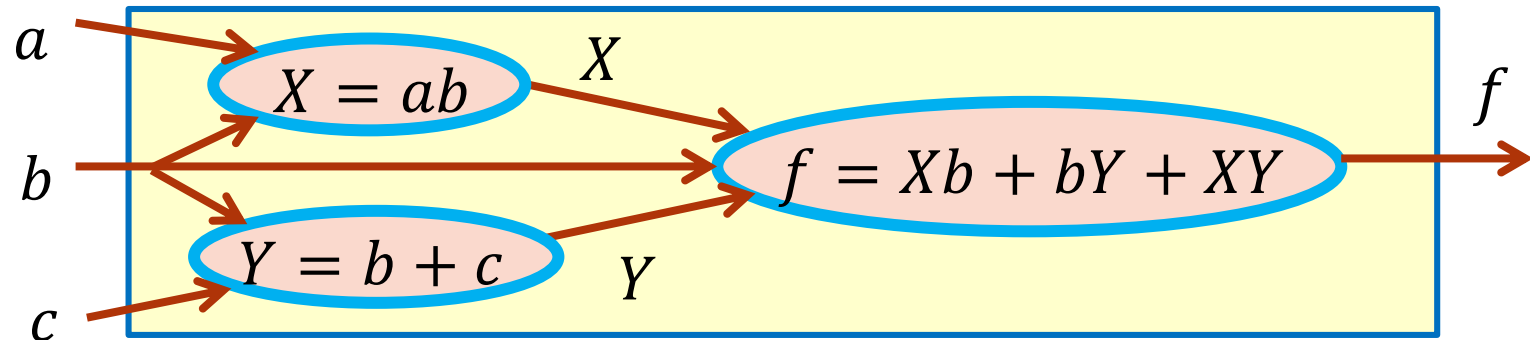

- Impossible patterns for (X, b, Y) are
 - $(1, 0, 0), (1, 0, 1)$ (From $X = ab$)
 - $(0, 1, 0), (1, 1, 0)$ (From $Y = b + c$)

Kmap for $f = Xb + bY + XY$

		Xb			
		00	01	11	10
Y	0			1	
	1		1	1	1




		Xb			
		00	01	11	10
Y	0		d	d	d
	1		1	1	d

f can be simplified
as $f = b$


Multi-level DCs: Informal Tour

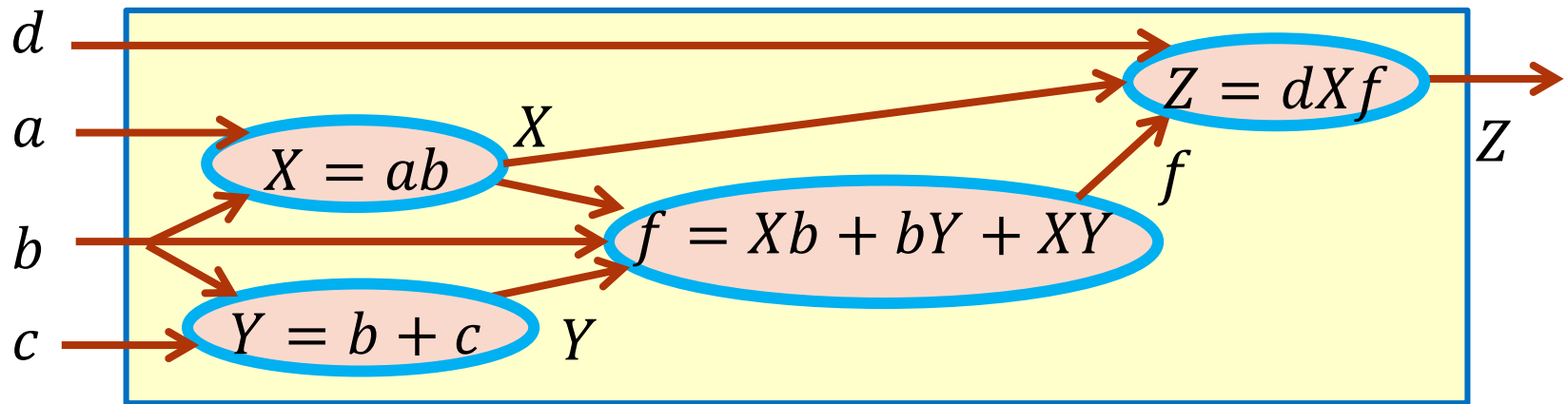- Now suppose f is not a **primary output**, Z is.



- Question**: when does the value of the output of node f actually **affect** the primary output Z ?
 - Or, said **conversely**: When does it **not matter** what f is?
 - Let's go look at patterns of (f, X, d) at node Z ...

When Is Z “Sensitive” to Value of f?

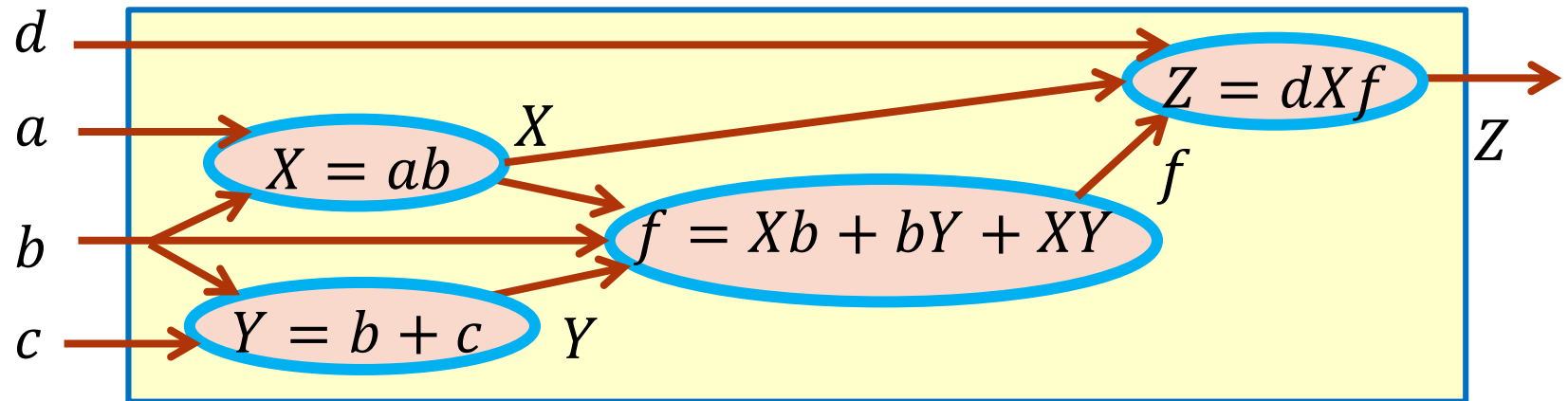


f	X	d	Z	Does f affect Z?
0	0	0	0	No
1	0	0	0	
0	0	1	0	No
1	0	1	0	
0	1	0	0	No
1	1	0	0	
0	1	1	0	Yes
1	1	1	1	

Can we use this information to find new patterns of (X, b, Y) to help us simplify f further?

YES!

When Is Z “Sensitive” to Value of f?

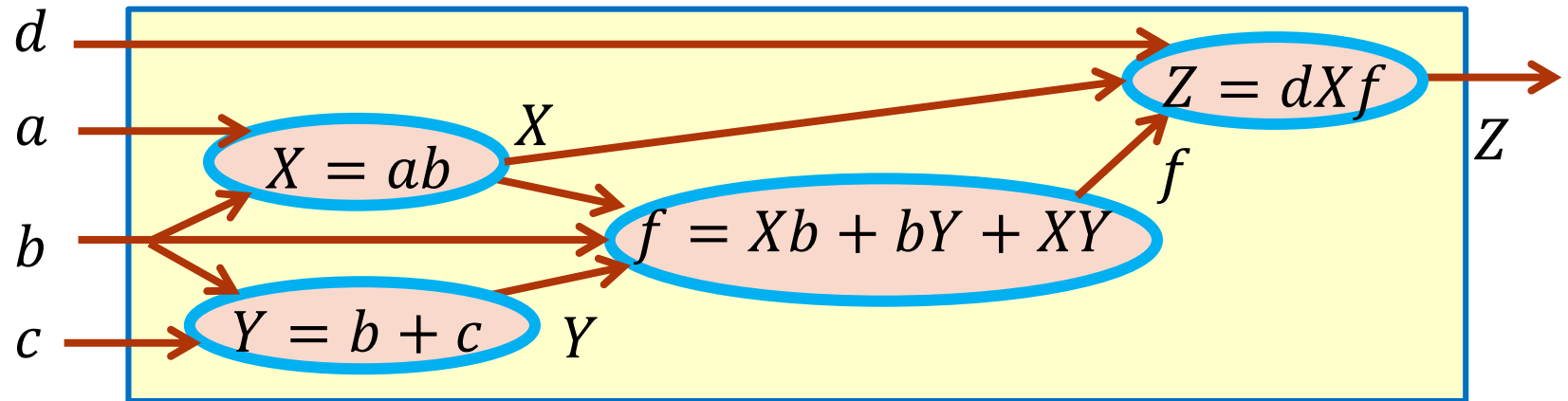


f	X	d	Z	Does f affect Z?
0	0	0	0	No
1	0	0	0	
0	0	1	0	No
1	0	1	0	
0	1	0	0	No
1	1	0	0	
0	1	1	0	Yes
1	1	1	1	

What patterns at **input to f** node (i.e., (X, b, Y)) are DCs, because those patterns make Z output **insensitive** to changes in f ?

$$(X, b, Y) = (0, -, -)$$

This means when $X = 0$, we can set f to any value – it **won't change** Z . So $(X, b, Y) = (0, -, -)$ is DC of f !

Multi-level DCs: Informal Tour

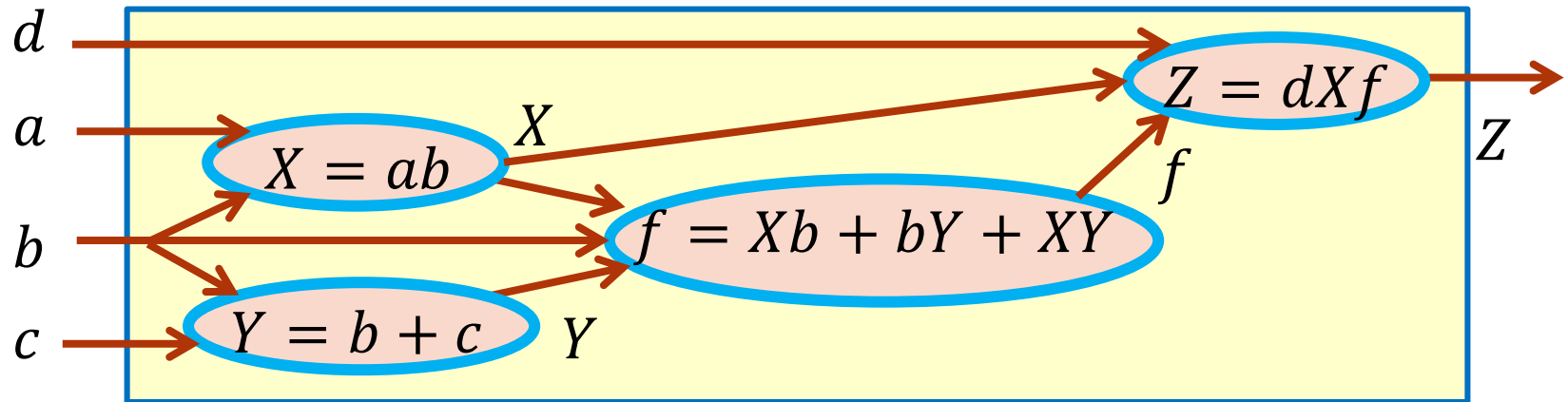

- So, we can use this **new** DC pattern $(0, -, -)$ to simplify f further...
 - ... with previous DC patterns $(1,0,0)$, $(1,0,1)$, $(0,1,0)$, $(1,1,0)$.

Kmap for $f = Xb + bY + XY$

		Xb			
		00	01	11	10
Y	0			1	
	1		1	1	1



With don't
cares

		Xb			
		00	01	11	10
Y	0	d	d	d	d
	1	d	d	1	d

f simplified as 1

Final Result: Multi-level DC Tour

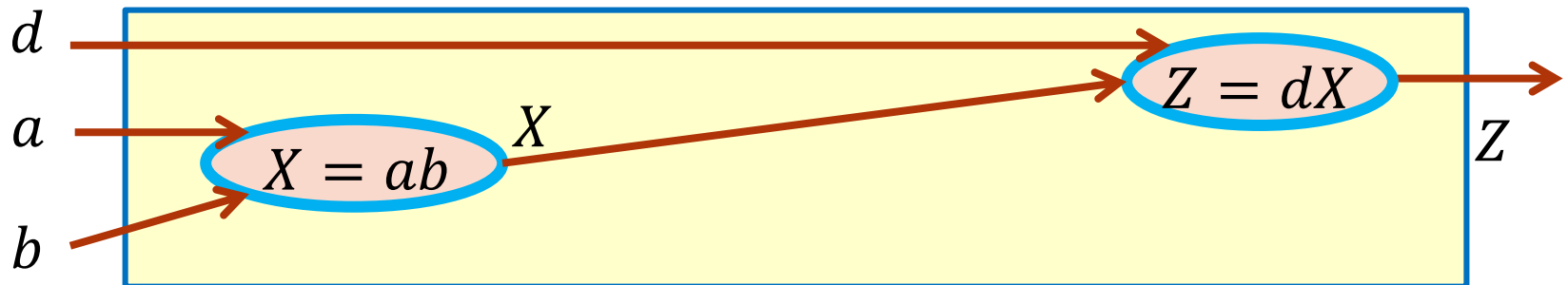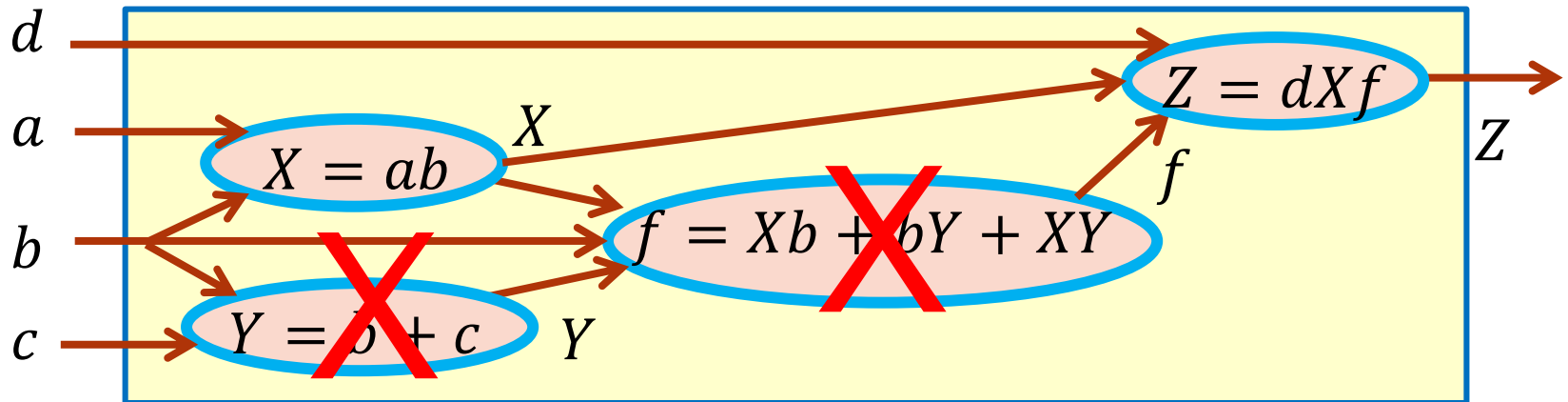- What happened to f ?
 - Due to network **context**, it disappeared ($f = 1$)!



Summary

- Don't Cares are **implicit** in the Boolean network model.
 - They arise from the **graph structure** of the multilevel Boolean network model itself.
- Implicit Don't Cares are **powerful**.
 - They can greatly help simplify the 2-level SOP structure of any node.
- Implicit Don't Cares require **computational work** to find.
 - For this example, we just “stared at the logic” to find the DC patterns.
 - We need some **algorithms** to do this automatically!
 - This is what we need to study next ...

Outline


- Implicit Don't Cares
 - Introduction
 - Method to Obtain them

3 Types of Implicit DCs

- **Satisfiability** don't cares: **SDCs**
 - Belong to the **wires** inside the Boolean logic network.
 - Used to compute **controllability** don't cares (below).
- **Controllability** don't cares: **CDCs**
 - Patterns that **cannot happen at inputs** to a network node.
- **Observability** don't cares: **ODCs**
 - Patterns that “**mask**” outputs.


Controllability don't cares: CDCs

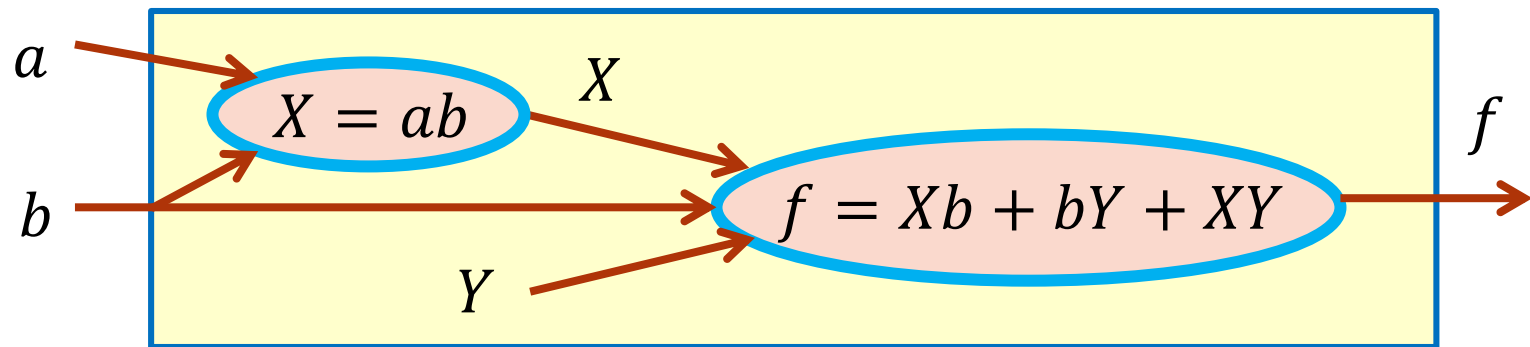- Patterns that **cannot happen at inputs** to a network node.
- **Example**
 - For node f , $(X, b, Y) = (1, 0, 0), (1, 0, 1)$ are CDCs.




Observability don't cares: ODCs

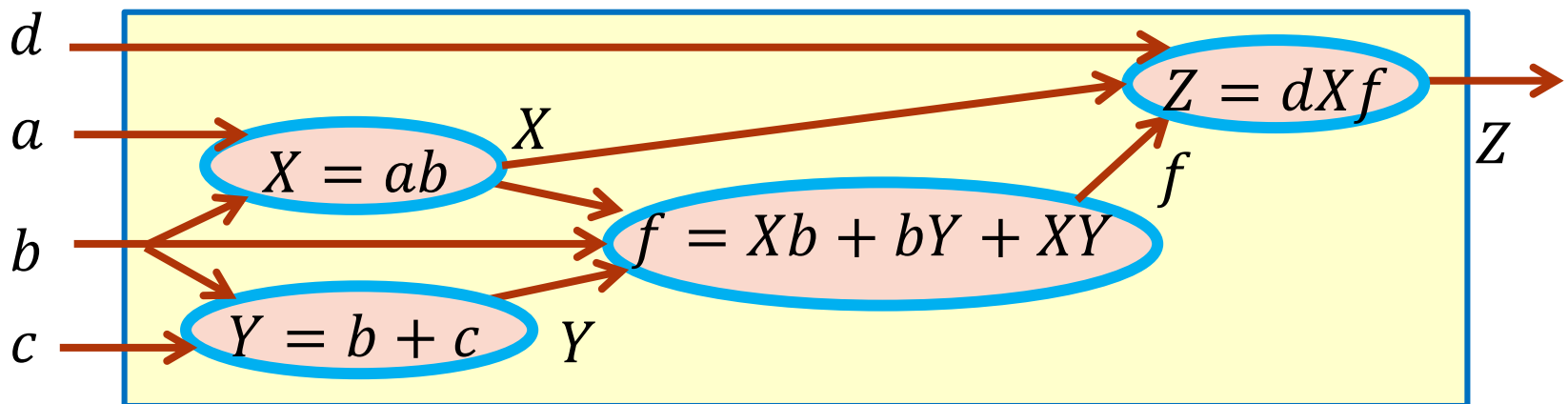- Input patterns to node that make primary outputs **insensitive** to output of the node.
 - Patterns that “**mask**” outputs.
- **Example**
 - For node f , $(X, b, Y) = (0, -, -)$ is ODC.



Background: Representing DC Patterns

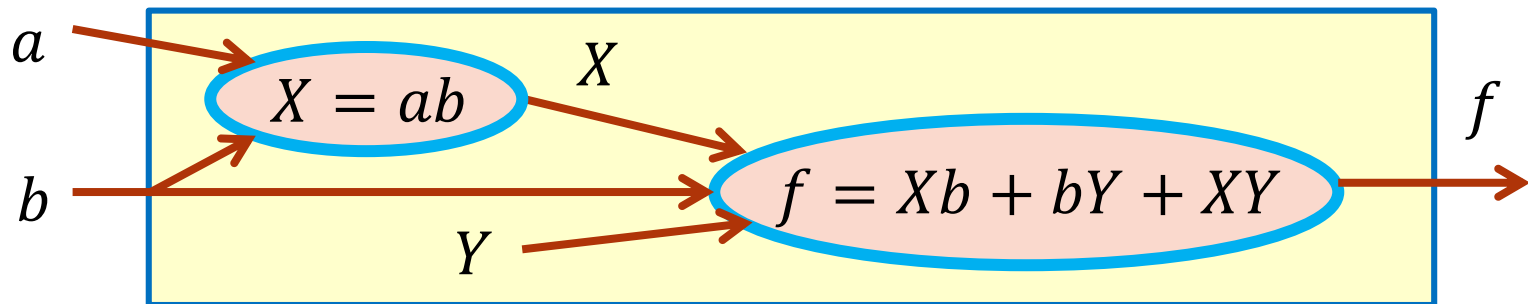- How shall we **represent** DC patterns at a node?
 - Answer: As a **Boolean function** that makes a 1 when the inputs are **these DCs**.
 - This is often called a **Don't Care Cover**.



Don't care pattern of $(X, b, Y) = (1, 0, 0), (1, 0, 1)$


The don't care cover is $X\bar{b}\bar{Y} + X\bar{b}Y = X\bar{b}$

Background: Representing DC Patterns

- So, each SDC, CDC, ODC is just another Boolean function, in this strategy.
- Why is it like this?
 - Because we can use all the other **computational Boolean algebra** techniques we know (e.g., BDDs), to **solve** for, and to **manipulate** the DC patterns.
 - This turns out to be hugely important to make the computation practical.


SDCs: They “Belong” to the Wires

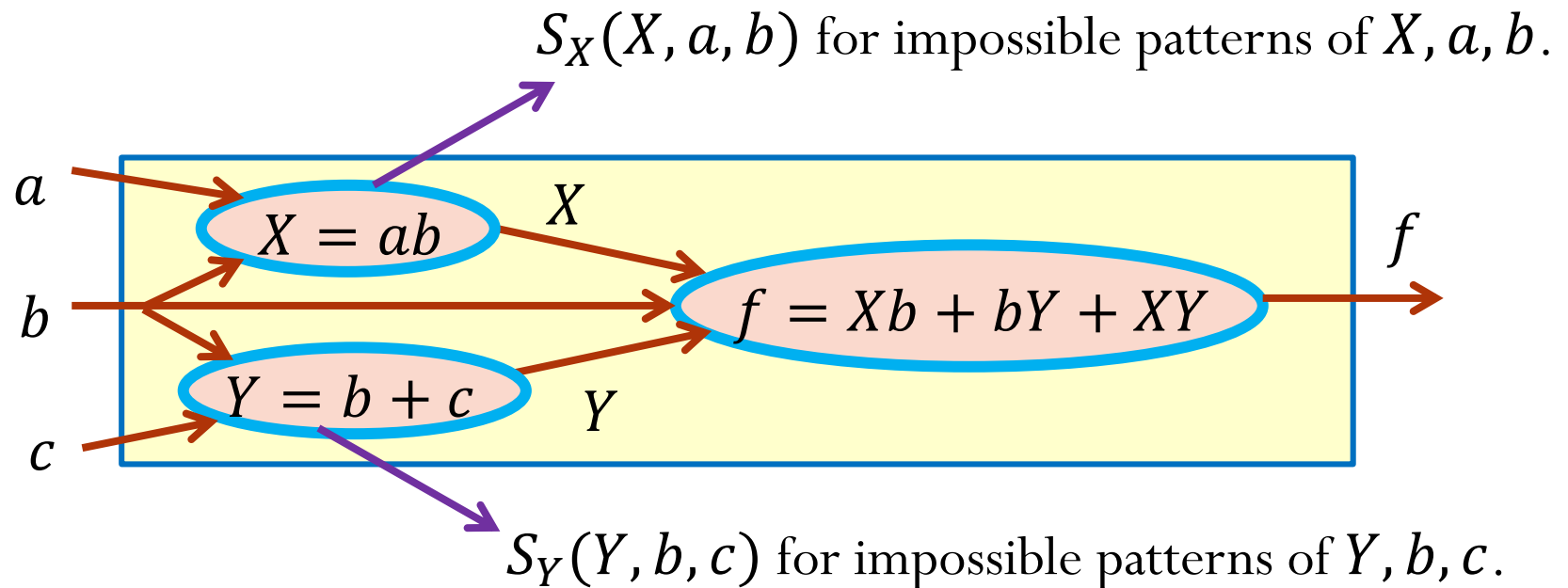- One SDC for every **internal wire** in Boolean logic network.
 - The SDC represents **impossible** patterns of **inputs to, and output of**, each node.
 - If the node function is F , with inputs a, b, c , write its SDC as: $S_F(F, a, b, c)$.




SDCs: How to Compute

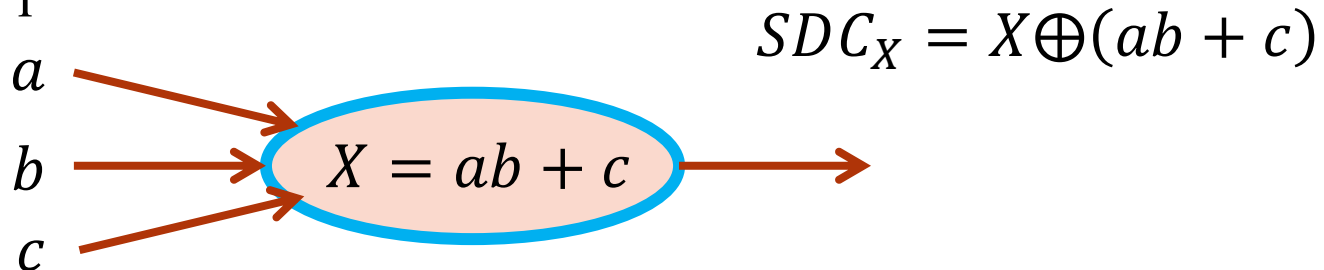- Compute an SDC for each output wire from each internal Boolean node.
- You want an expression that is 1 when output X **does not equal** the Boolean expression for X .
 - This is just: $X \oplus (\text{expression for } X)$
 - Note #1: expression for X doesn't have X in it!
 - Note #2: this is the **complement** of the gate consistency function from SAT.
- Example



SDCs: Example

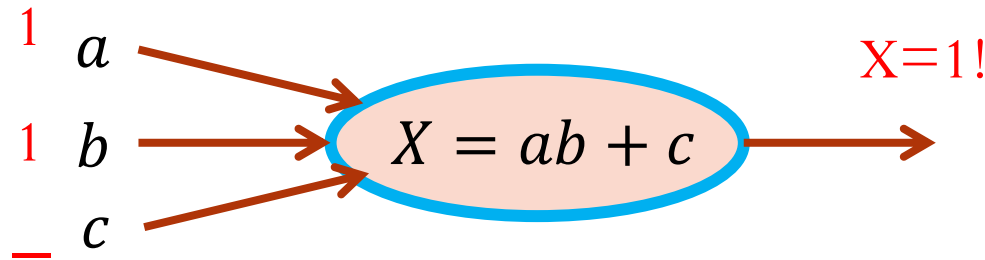

- $SDC_X = X \oplus (ab + c) = \bar{X}ab + \bar{X}c + X\bar{a}\bar{c} + X\bar{b}\bar{c}$




One **impossible pattern**: $Xabc = 011 -$

SDCs: Summary

- SDCs are associated with every **internal wire** in Boolean logic network.
 - SDCs explain **impossible patterns** of input to, and output of, each node.
 - SDCs are easy to compute.
- SDCs alone are **not** the Don't Cares used to simplify nodes.
 - We use SDCs to **build CDCs**, which give impossible patterns at input of nodes.


How to Compute CDCs?

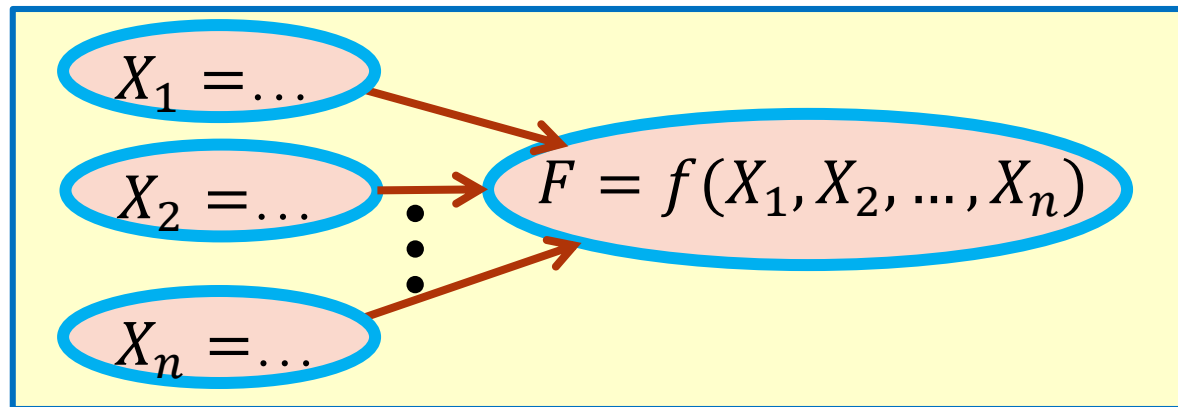- Computational recipe:
 1. Get all the **SDCs** on the wires **input to** this node in Boolean logic network.
 2. **OR** together all these SDCs.
 3. **Universally Quantify** away all variables that are **NOT** used inside this node.



$$CDC_F(X_1, \dots, X_n) = (\forall \text{ vars not used in } F) \left[\sum_{\text{input } X_i \text{ to } F} SDC_{X_i} \right]$$

How to Compute CDCs?

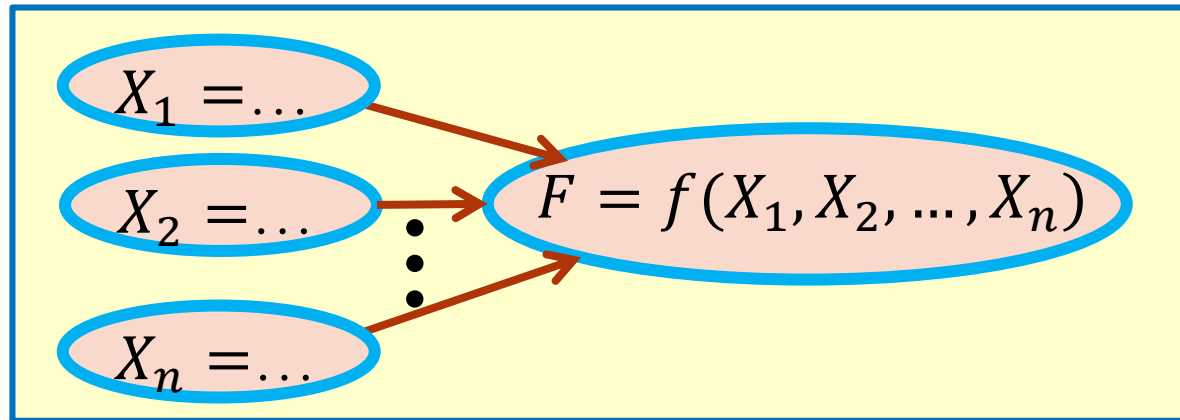

$$CDC_F(X_1, \dots, X_n) = (\forall \text{ vars not used in } F) \left[\sum_{\text{input } X_i \text{ to } F} SDC_{X_i} \right]$$

- **Result**: Inputs that let $CDC_F = 1$ are **impossible patterns** at input to node!


CDCs: Why Does This Work?

$$CDC_F(X_1, \dots, X_n) = (\forall \text{ vars not used in } F) \left[\sum_{\text{input } X_i \text{ to } F} SDC_{X_i} \right]$$

- Roughly speaking...
 - SDC_{X_i} 's explain all the impossible patterns involving X_i wire input to the F node.
 - **OR** operation is just the “**union**” of all these impossible patterns involving X_i 's.
 - **Universal Quantification** removes variables **not** used by F , and does so in the right way: we want patterns that are impossible **FOR ALL** values of these removed variables.

Compute CDCs: Example


Obtain CDCs for the node f

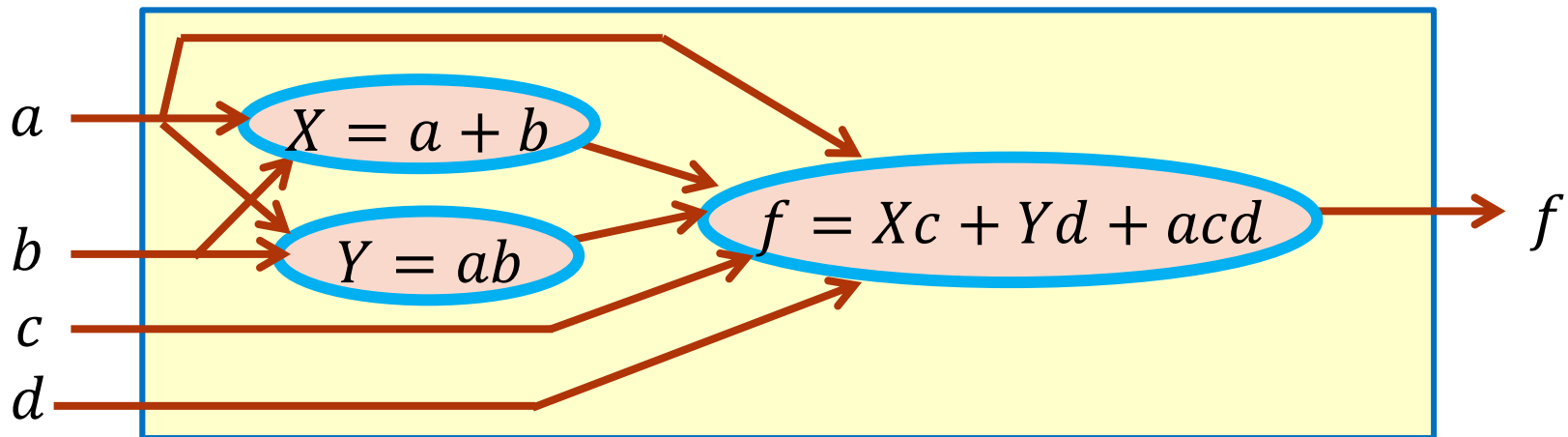


$$CDC_f(X_1, \dots, X_n) = (\underbrace{\forall \text{ vars not used in } f}_{\text{This is } b}) \left[\underbrace{\sum_{\text{input } X_i \text{ to } f} SDC_{X_i}}_{\text{Input variables to } f \text{ are } a, c, d, X, Y} \right]$$

Compute CDCs: Example

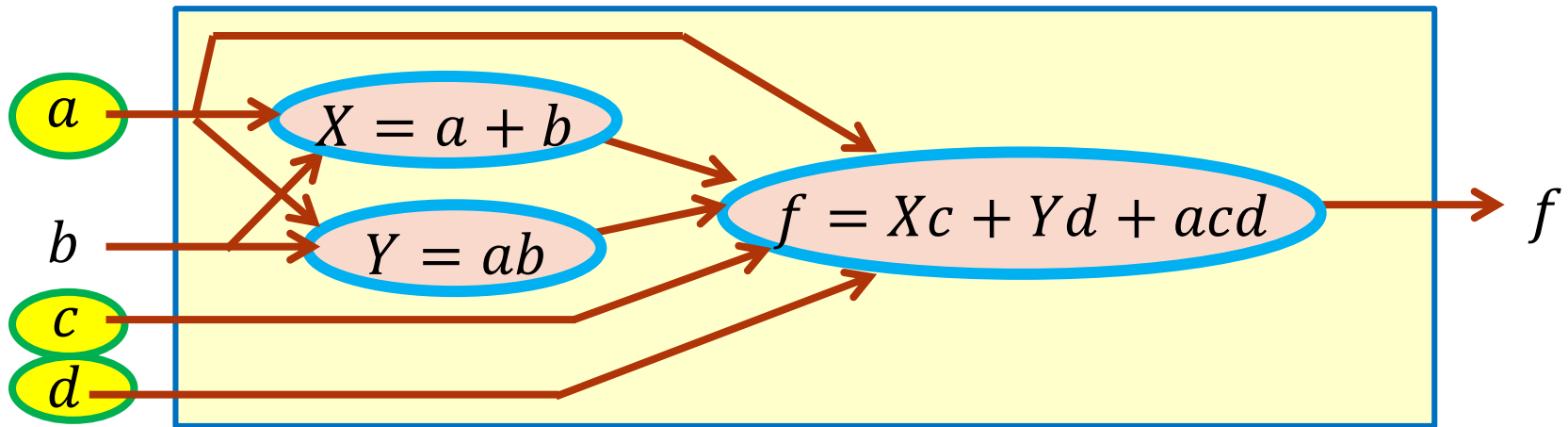- What about SDCs on **primary inputs**?
 - They are just 0.
 - Why? $SDC_a = a \oplus (\text{expression for } a) = a \oplus a = 0$.
- **Thus**: SDCs on primary inputs have no impact on OR. We can **ignore primary inputs**.




Compute CDCs: Example

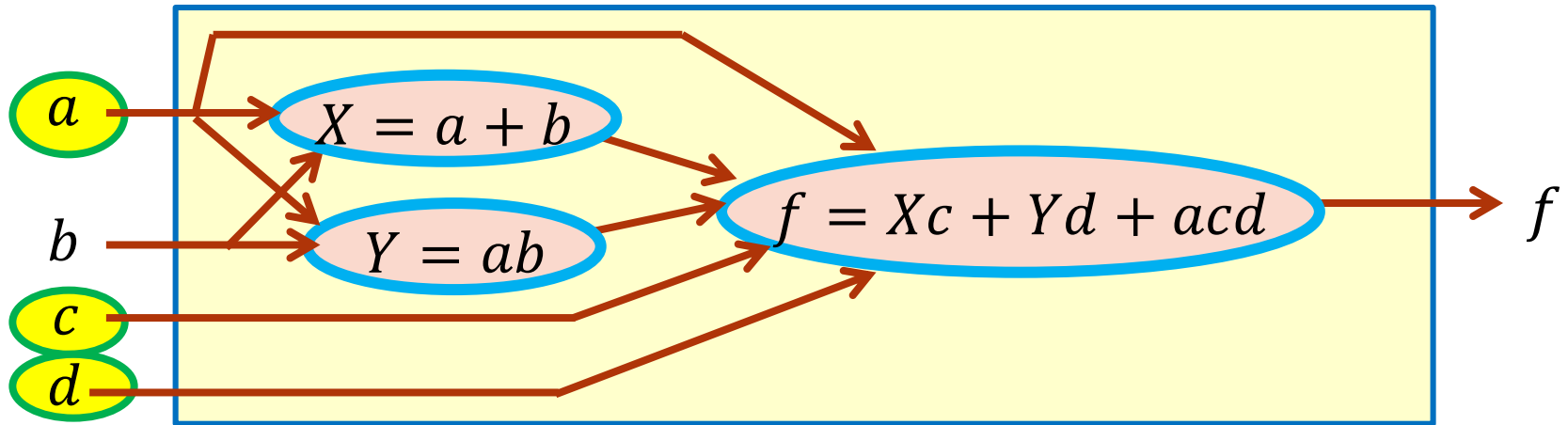

- Since we ignore primary inputs, we have ...

$$CDC_f(X_1, \dots, X_n) = (\underbrace{\forall \text{ vars not used in } f}_{\text{This is } b}) \left[\underbrace{\sum_{\text{input } X_i \text{ to } f} SDC_{X_i}}_{\text{Only } X, Y} \right]$$


Compute CDCs: Example

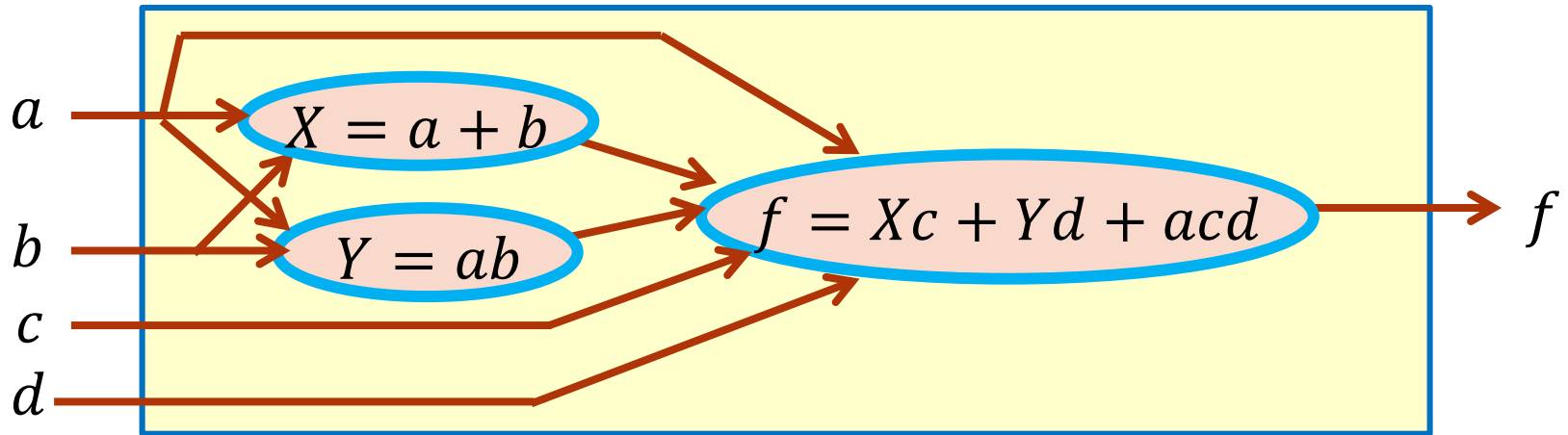

- Thus, we have:

$$\begin{aligned}
 CDC_f &= (\forall b)[SDC_X + SDC_Y] = (\forall b)[[X \oplus (a + b)] + [Y \oplus ab]] \\
 &= [[X \oplus (a + b)] + [Y \oplus ab]]_{b=1} \cdot [[X \oplus (a + b)] + [Y \oplus ab]]_{b=0} \\
 &= [\bar{X} + (Y \oplus a)] \cdot [(X \oplus a) + Y] = \bar{X}a + Y\bar{a}
 \end{aligned}$$


Compute CDCs: Example

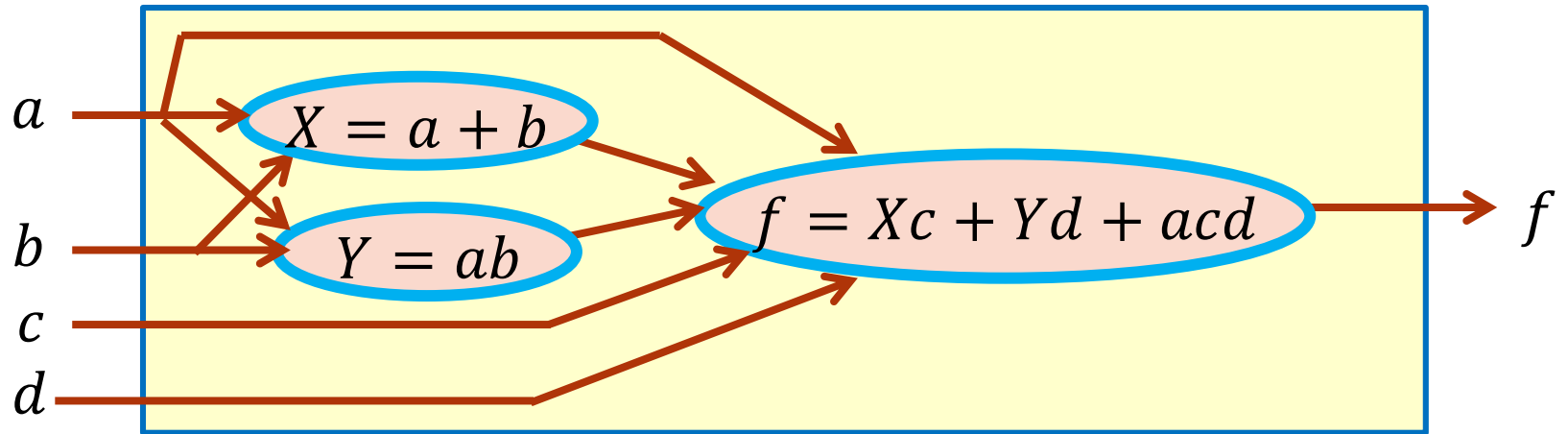

- $CDC_f = \bar{X}a + Y\bar{a}$
- Does it **make sense**?
 - From CDC_f , **impossible patterns** are
 - $(X, a) = (0, 1) \quad a = 1 \Rightarrow X = 1$
 - $(Y, a) = (1, 0) \quad a = 0 \Rightarrow Y = 0$


How to Handle External CDCs?

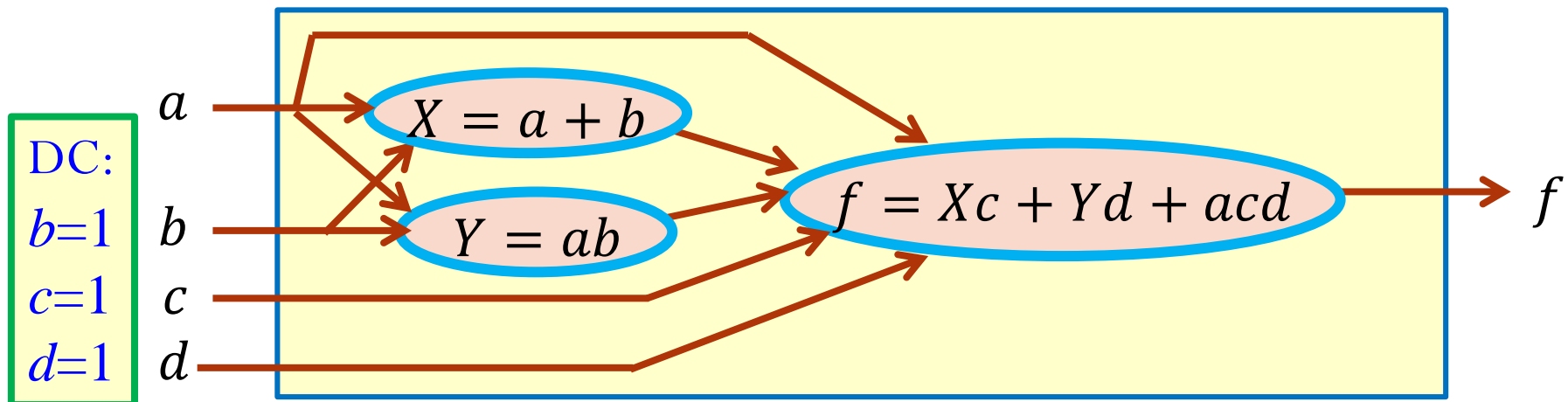- What if there are **external DCs** for primary inputs a, b, c, d for which we just **don't care** what f does?
 - **Answer:** Just **OR** these DCs in $(\sum SDC_i)$ part of CDC expression.
 - Represent these DCs as a **Boolean function** that makes a 1 when the inputs are **these DCs**.



Handling External CDCs: Example

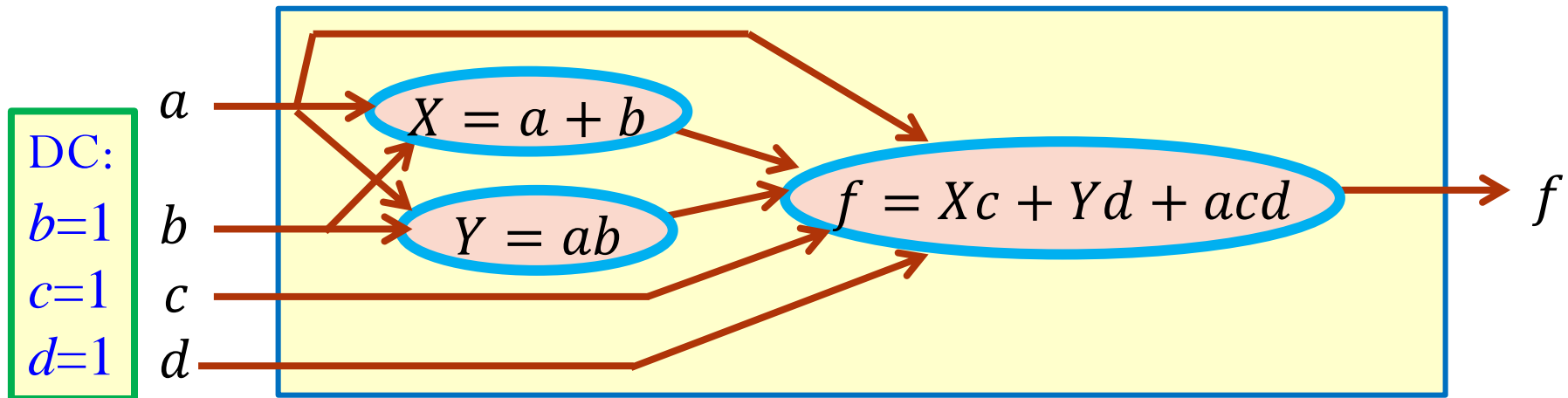
- Suppose $(b, c, d) = (1, 1, 1)$ cannot happen.
 - How to compute CDC_f now?



$$CDC_f = (\forall b) \left([X \oplus (a + b)] + [Y \oplus ab] + \underbrace{bcd} \right)$$

External DCs as a **Boolean function** that makes a 1 when the pattern is **impossible**.

Handling External CDCs: Example

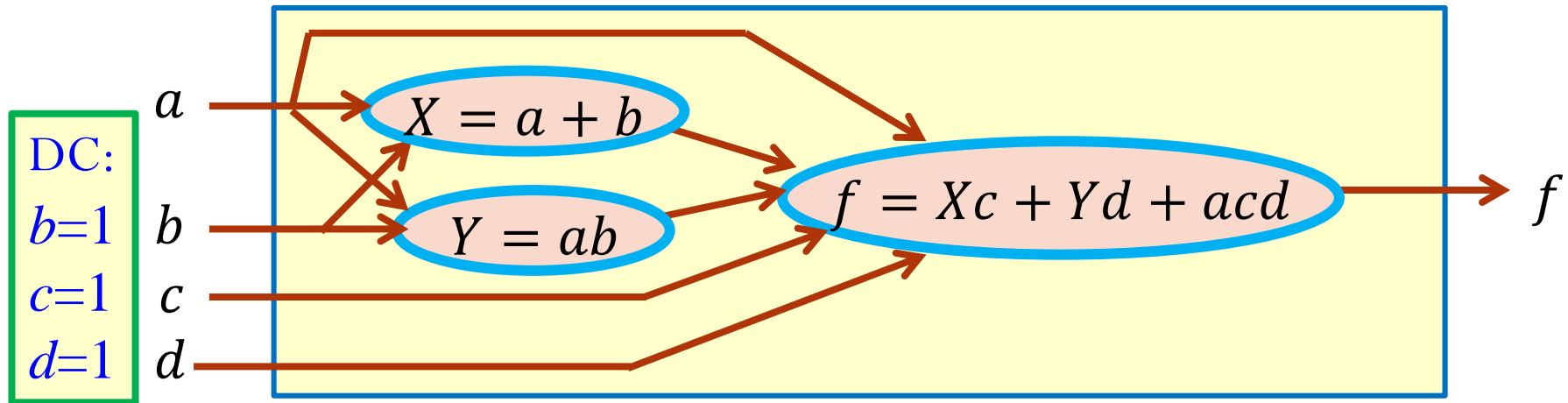

$$CDC_f = (\forall b)[[X \oplus (a + b)] + [Y \oplus ab] + bcd]$$

$$= \bar{X}a + Y\bar{a} + \bar{a}cdX + cdY$$

- **New impossible patterns** are

Make sense?

- $(a, c, d, X) = (0, 1, 1, 1)$ $a = 0 \ \&\& \ X = 1 \Rightarrow b = 1$

Thus, $b = c = d = 1$

- $(c, d, Y) = (1, 1, 1)$ $Y = 1 \Rightarrow b = 1$

Thus, $b = c = d = 1$

CDCs: Summary


- CDCs give **impossible patterns** at input to node F – use as DCs.
 - Impossible because of the network structure of the nodes **feeding** node F .
 - CDCs can be computed mechanically from **SDCs** on wires input to F .
 - **Internal local CDCs**: computed just from SDCs on wires into F .
 - **External global CDCs**: include DC patterns in the SDC sum.

CDCs: Summary (cont.)

- But CDCs are still **not all** the Don't Cares available to simplify nodes.
 - CDC_F derived from the structure of nodes “**before**” node F .
 - We need to look at DCs that derive from nodes “**after**” node F .
 - These are nodes between the **output** of F and **primary outputs** of the network.
 - These are ODCs.

Observability Don't Cares (ODCs)


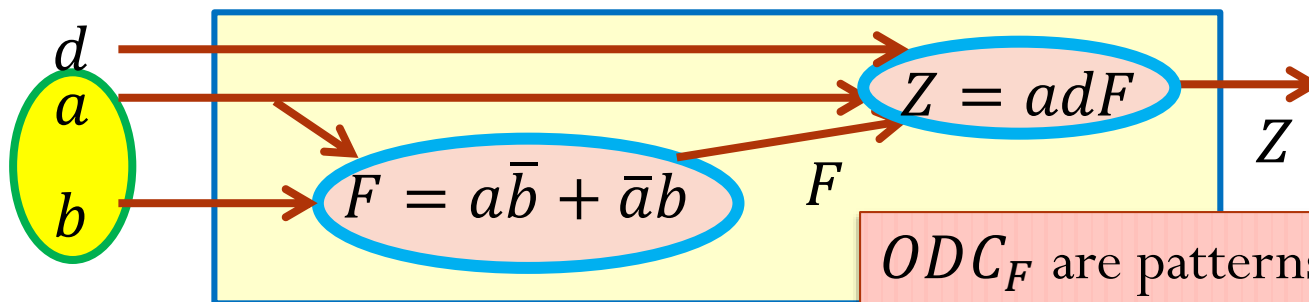
- **ODCs**: patterns that **mask** a node's output at primary output (PO) of the network.
 - So, these are **not** impossible patterns – these patterns **can occur** at node input.
 - These patterns make this node's output **not observable at primary output**.
 - “**Not observable**” for an input pattern means: Boolean value of node output **does not affect** ANY primary output.




ODC_F are patterns of (a, b) that make Z **insensitive** to F 's value.

Primary Output Insensitive to F

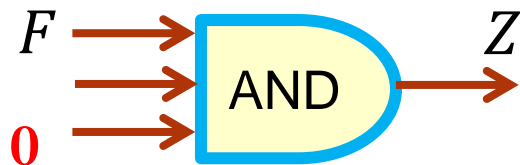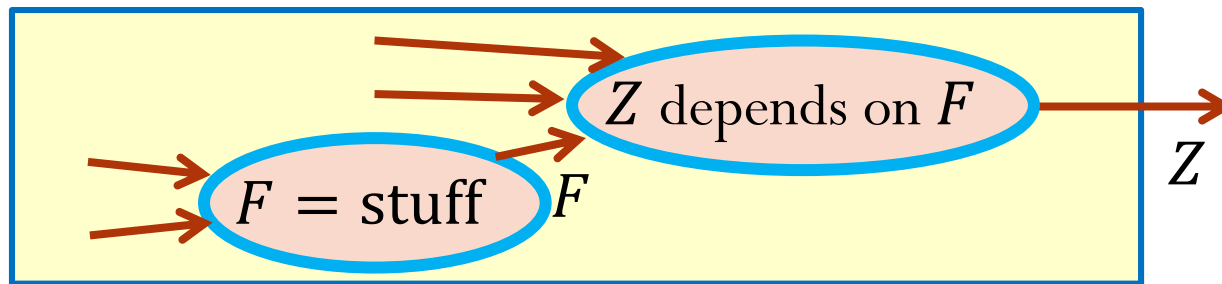- When is primary output Z **insensitive** to internal variable F ?
 - Means Z **independent** of value of F , given other inputs to Z .



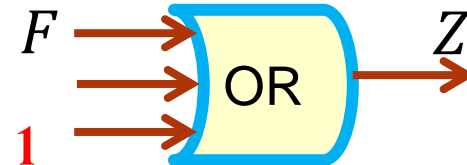
Z **insensitive** to F if
another input = 0



Z **insensitive** to F if
another input = 1

How about the general case?

Recall: Boolean Difference

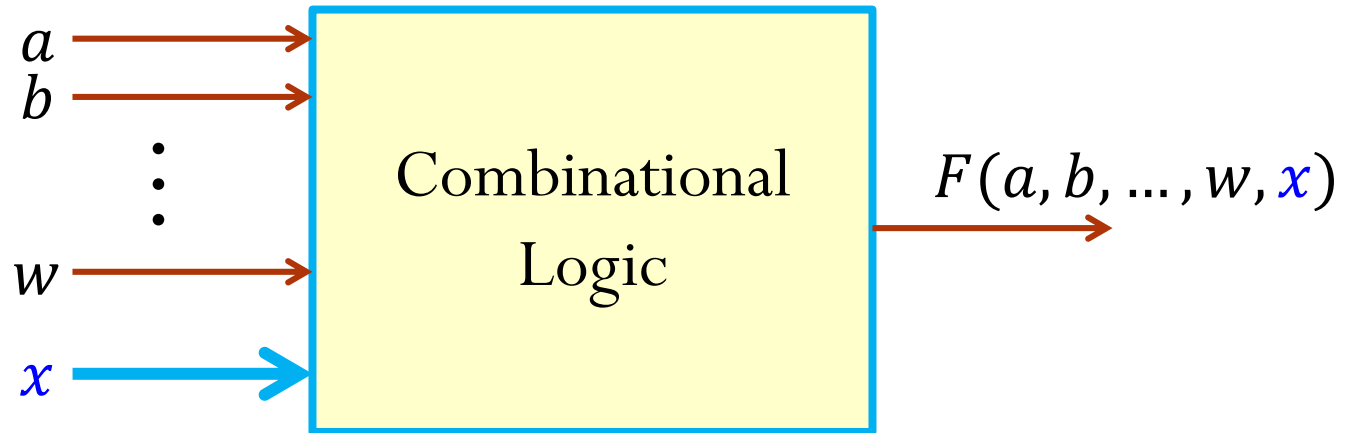


- What does **Boolean difference**
 $\partial F(a, b, \dots, w, x) / \partial x = F_x \oplus F_{\bar{x}} = 1$ mean?
 - If you apply an input pattern (a, b, \dots, w) that makes $\partial F / \partial x = 1$, then **any change** in x will **force a change** in output F .
- What makes output F **sensitive** to input x ?
 - **Answer**: Any pattern that makes $\frac{\partial F}{\partial x} = F_x \oplus F_{\bar{x}} = 1$.

Z Insensitive to F

- When is primary output Z **insensitive** to internal variable F ?
 - Answer: when inputs (other than F) to Z make cofactors $Z_F = Z_{\bar{F}}$.
 - **Make sense**: if cofactors with respect to F are **same**, Z does not depend on F !
- How to find when cofactors are the same?
 - Answer: Solve for $Z_F \oplus Z_{\bar{F}} = 1$
 - Note: $Z_F \oplus Z_{\bar{F}} = 1 \Rightarrow \overline{Z_F \oplus Z_{\bar{F}}} = 1 \Rightarrow \frac{\partial Z}{\partial F} = 1$

How to Compute ODCs?

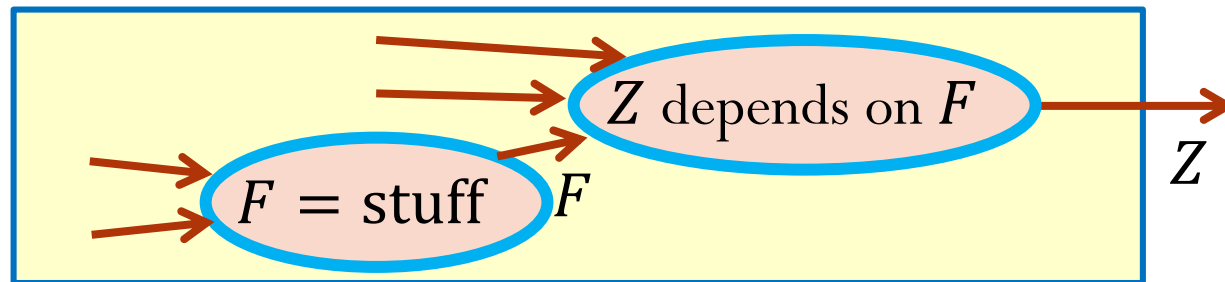- A nice computational recipe:
 1. **Compute** $\overline{\partial Z / \partial F}$. Any patterns that make $\overline{\partial Z / \partial F} = 1$ **mask** output F for Z .
 2. **Universally Quantify** away all variables that are **NOT** inputs to the F node.




$$ODC_F(X_1, \dots, X_n) = (\forall \text{ vars not used in } F) \left[\overline{\partial Z / \partial F} \right]$$

Result: Inputs that let $ODC_F = 1$ **mask** output F for Z , i.e., make Z **insensitive** to F .

Compute ODCs: Example

- Obtain the ODCs for node F .

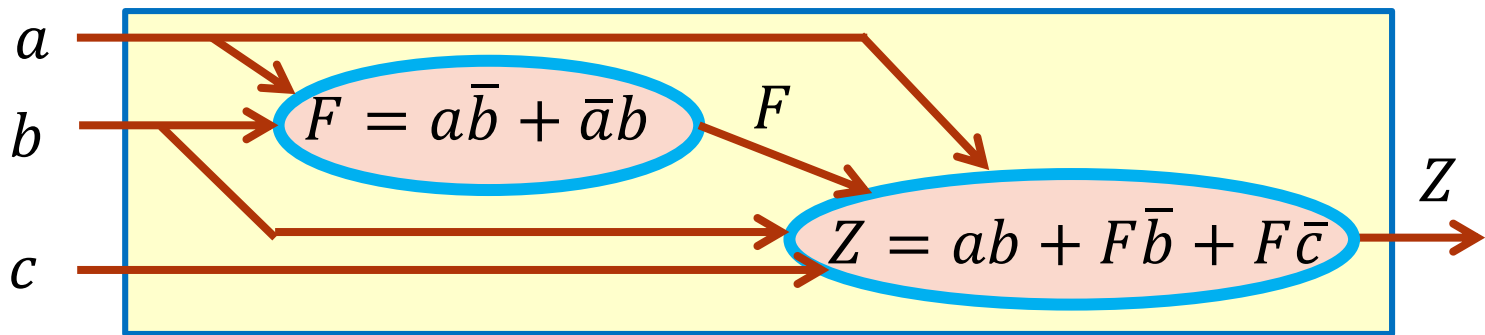


$$ODC_F(\underbrace{X_1, \dots, X_n}_{\text{They are } a, b}) = (\underbrace{\forall \text{ vars not used in } F}_{\text{This is } c}) \left[\overline{\partial Z / \partial F} \right]$$

$$= (\forall c) \left[\overline{(ab + F\bar{b} + F\bar{c})_{F=1} \oplus (ab + F\bar{b} + F\bar{c})_{F=0}} \right]$$

$$= (\forall c) \left[\overline{(a + \bar{b} + \bar{c}) \oplus (ab)} \right] = ab$$


Check: Does this ODC Make Sense?

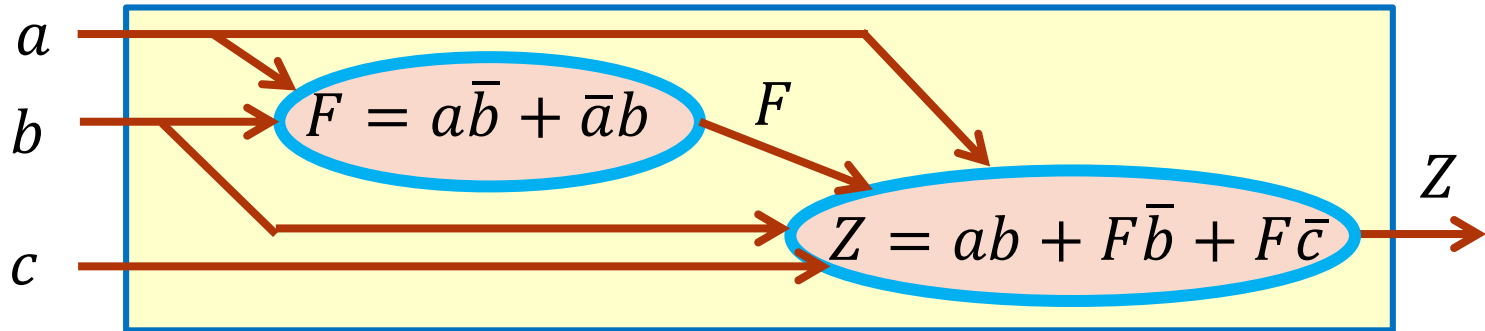

- $ODC_F = ab$
 - ODC pattern is $(a, b) = (1, 1)$
- Make sense! Because when $(a, b) = (1, 1)$, $Z = 1$ independent of F .

ODCs: More General Case

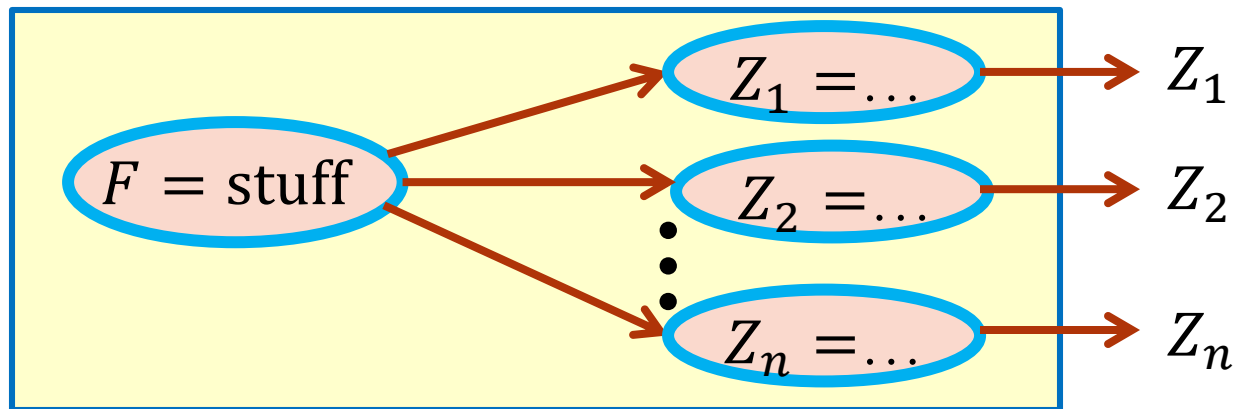- Question: what if F feeds to **many** primary outputs?
- Answer: Only patterns that are **unobservable** at **ALL** outputs can be ODCs.



- Computational recipe:


$$ODC_F = (\forall \text{ vars not used in } F) \left[\underbrace{\prod_{\text{Output } Z_i} \overline{\partial Z_i / \partial F}} \right]$$

AND all n differences for each output Z_i .

ODCs: Summary


- ODCs give input patterns of node F that **mask** F at **primary outputs**.
 - **Not** impossible patterns – they **can occur**.
 - Don't cares because primary output “**doesn't care**” what F is, for these patterns.
 - ODCs can be computed mechanically from $\overline{\partial Z_i / \partial F}$ on all outputs connected to F .
- CDCs + ODCs give the “**full**” don't care set used to simplify F .
 - With these patterns, you can call something like ESPRESSO to simplify F .

Multi-Level Don't Cares: Are We Done?

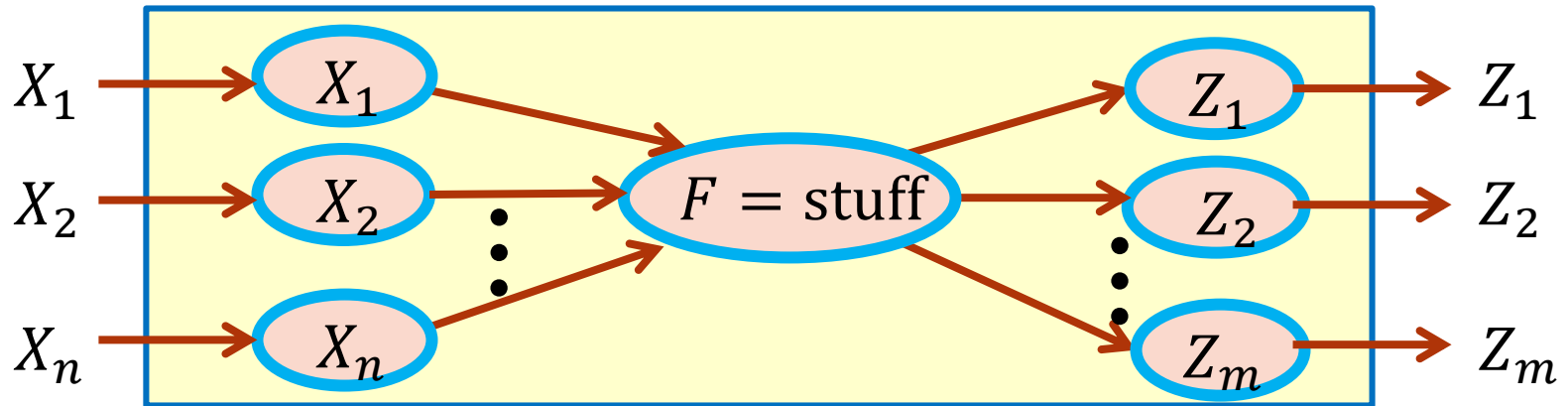

- Yes, if your networks look **just like above**.
 - More precisely, if you only want to get CDCs from nodes **immediately** “before” you.
 - And if you only want to get ODCs for **one layer of nodes** between you and output.

Don't Cares, In General

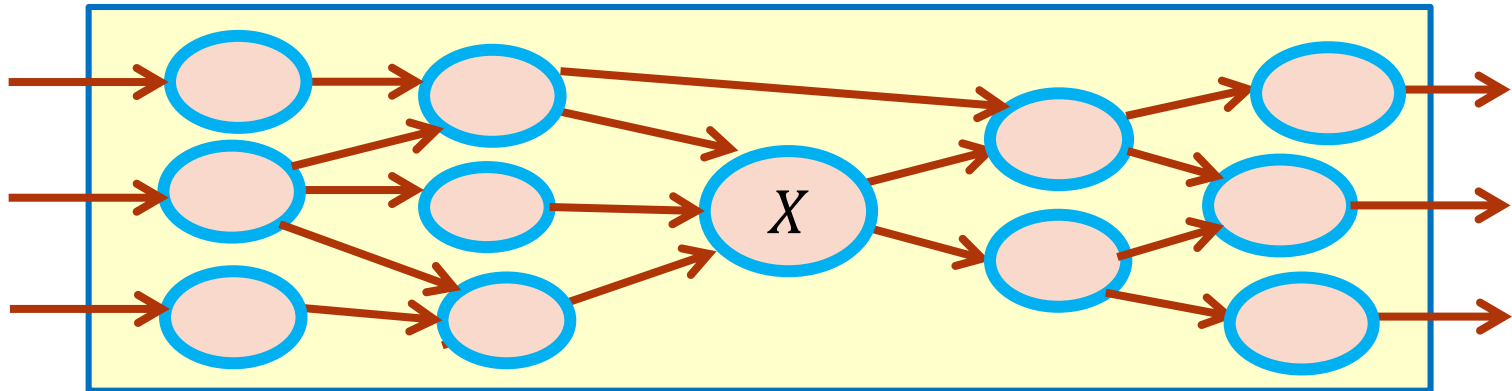

- However, **real** multi-level logic looks like this!
 - CDCs are function of **all nodes** “before” X .
 - ODCs are function of **all nodes** between X and any output.
 - In general, we can **never get all** the DCs for node X in a big network.
 - Representing all this stuff can be **explosively** large, even with BDDs

Summary: Getting Network DCs

- How we really do it? generally **do not get all** the DCs.
 - Lots of tricks that trade off effort (time, memory) with quality (how many DCs).
 - Example: Can just extract “**local CDCs**”, which requires looking at outputs of **immediate precedent** vertices and computing from the SDC patterns, which is easy.
 - There are also algorithms that walk the network to compute more of the CDC and ODC set for X, but these are more **complex**.
- For us, knowing these “limited” DC recipes is **sufficient**.